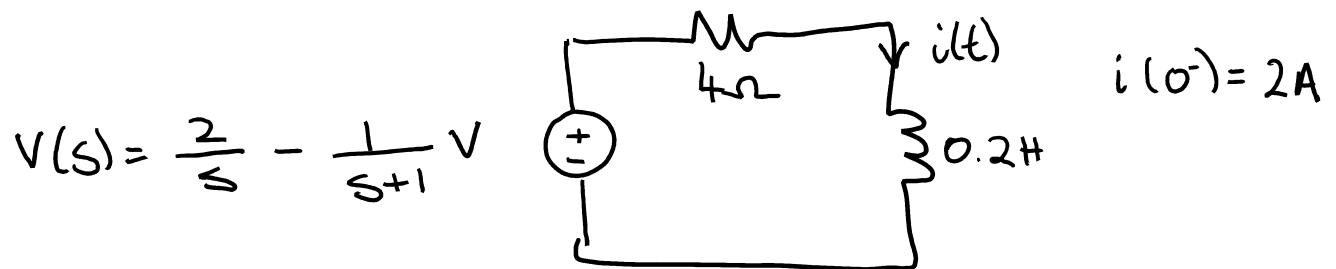


## At Tutorial 8 – Marked Question (9<sup>th</sup> August 2019)

### Chapter 14 Ex 48a: Laplace Transformations

For the circuit below, write the s-domain KVL equation in terms of  $I(s)$ . Rearrange and simplify the equation to get an s-domain expression for  $I(s)$ .



## At Tutorial 8 – Unmarked Questions (9<sup>th</sup> August 2019)

### Chapter 14, Ex 27: Laplace Transformations

Using the Laplace transform tables, determine  $F(s)$  if  $f(t)$  is equal to:

- a)  $3u(t - 2)$
- b)  $3e^{-2t}u(t) + 5u(t)$
- c)  $\delta(t) + u(t) - tu(t)$
- d)  $5\delta(t)$


### Chapter 14, Ex 35: Laplace Transforms

Determine the inverse transform of  $F(s)$  equal to:

- a)  $5 + \frac{5}{s^2} - \frac{5}{(s+1)}$
- b)  $\frac{1}{s} + \frac{5}{0.1s+4} - 3$
- c)  $-\frac{1}{2s} + \frac{1}{(0.5s)^2} + \frac{4}{(s+5)(s+5)} + 2$
- d)  $\frac{4}{(s+5)(s+5)} + \frac{2}{s+1} + \frac{1}{s+3}$
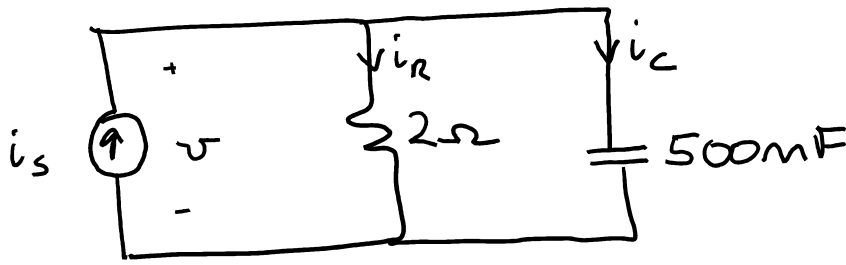
### Chapter 14, Ex 46: Laplace Transformations

For the circuit below, the initial voltage across the capacitor is  $v(0^-) = 1.5$  V and the current source is  $i_s = 700u(t)$  mA.



- Write the differential equation which arises from KCL, in terms of the nodal voltage  $v(t)$ .
- Take the Laplace transform of the differential equation.
- Determine the frequency-domain representation of the nodal voltage

### Chapter 14, Ex 61: Impedance

The voltage  $v(t) = 8e^{-2} u(t)$  V is applied to a two-terminal device. Your assistant misunderstands you and only records the  $s$ -domain current which results. Determine what type of element it is and its value if  $I(s)$  is equal to:

- $\frac{1}{s+2}$  A
- $\frac{4}{s(s+2)}$  A

### Chapter 14, Ex 64a: Time-Domain Mesh Analysis, LT, Inverse LT

Referring to the circuit below and keeping the circuit in the time-domain, develop an expression for  $I_C(s)$ , then determine  $i_C(t)$  for  $t > 0$  if  $i_s(t) = 2u(t+2)$  A and  $v_s(t) = 2u(t)$  V. HINTS: You can work out the initial conditions using techniques from term 2. Use mesh analysis in the time domain for  $t > 0$ . Voltage drop across a capacitor is  $v_C(t) = \frac{1}{C} \int_{t_0}^t i(T) dT + v_C(t_0)$ .

