

Name:

Student ID:

Pre-tutorial 8 Questions (to be attempted before class on August 9th, 2019)

Chapter 14, Ex 21: Laplace Transforms

Using the one-sided Laplace transform equation, calculate (showing intermediate steps) the Laplace transform of the following:

d) $2.1u(t)$

$$\begin{aligned} F(s) &= \int_{0^-}^{\infty} e^{-st} 2.1u(t) dt \\ &= 2.1 \int_{0^-}^{\infty} e^{-st} dt \\ &= 2.1 \left[-\frac{1}{s} e^{-st} \right]_{0^-}^{\infty} \\ &= 2.1 \left[0 - -\frac{1}{s} \right] \\ &= \frac{2.1}{s} \end{aligned}$$

c) $5u(t-2) - 2u(t)$

$$\begin{aligned} F(s) &= \int_{0^-}^{\infty} e^{-st} (5u(t-2) - 2u(t)) dt \\ &= 5 \int_2^{\infty} e^{-st} dt - 2 \int_{0^-}^{\infty} e^{-st} dt \\ &= 5 \left[-\frac{1}{s} e^{-st} \right]_2^{\infty} - 2 \left[-\frac{1}{s} \right]_{0^-}^{\infty} \\ &= 5 \left[0 - -\frac{1}{s} e^{-2s} \right] - 2 \left[0 - -\frac{1}{s} \right] \\ &= \frac{5}{s} e^{-2s} - \frac{2}{s} \end{aligned}$$

Chapter 14, Ex 59: IVT and FVT

Apply the initial- or final-value theorems as appropriate to determine $f(0^+)$ and $f(\infty)$ for the following functions:

a) $\frac{s+2}{s^2+8s+4}$

$$\begin{aligned} f(0^+) &= \lim_{s \rightarrow \infty} s F(s) \\ &= \lim_{s \rightarrow \infty} \frac{s^2 + 2s}{s^2 + 8s + 4} \end{aligned}$$

$$= \lim_{s \rightarrow \infty} \frac{1 + 2/s}{1 + 8/s + 4/s^2}$$

$$= 1$$

For FVT, need to check poles:

$$\text{poles} \Rightarrow s^2 + 8s + 4 = 0$$

$$s = \frac{-8 \pm \sqrt{8^2 - 4 \times 4}}{2}$$

$$= -0.54, -7.46 \quad \checkmark \text{ all in LHP}$$

$$f(\infty) = \lim_{s \rightarrow \infty} \frac{s^2 + 2s}{s^2 + 8s + 4}$$

$$= 0/4$$

$$= 0$$

c) $\frac{4s^2 + 1}{(s+1)^2(s+2)^2}$

$$f(0^+) = \lim_{s \rightarrow \infty} sF(s)$$

$$= \lim_{s \rightarrow \infty} \frac{4s^3 + s}{(s+1)^2(s+2)^2}$$

$$= \lim_{s \rightarrow \infty} \frac{4s^3 + s}{(s^2 + 2s + 1)(s^2 + 4s + 4)}$$

$$= \lim_{s \rightarrow \infty} \frac{4s^3 + s}{s^4 + 4s^3 + 4s^2 + 2s^3 + 8s^2 + 8s + s^2 + 4s + 4}$$

$$= \lim_{s \rightarrow \infty} \frac{4s^3 + s}{6s^4 + 6s^3 + 13s^2 + 12s + 4}$$

$$= 0$$

check poles for FVT. Poles $\Rightarrow (s+1)^2(s+2)^2 = 0$

$$s = -1, -2$$

(repeated)

all LHP, \therefore OK

$$f(\infty) = \lim_{s \rightarrow 0} \frac{4s^3 + s}{s^4 + 6s^3 + 13s^2 + 12s + 4}$$


$$= 0/4$$

$$= 0$$

At Tutorial 8 – Marked Question (9th August 2019)

Chapter 14 Ex 48a: Laplace Transformations

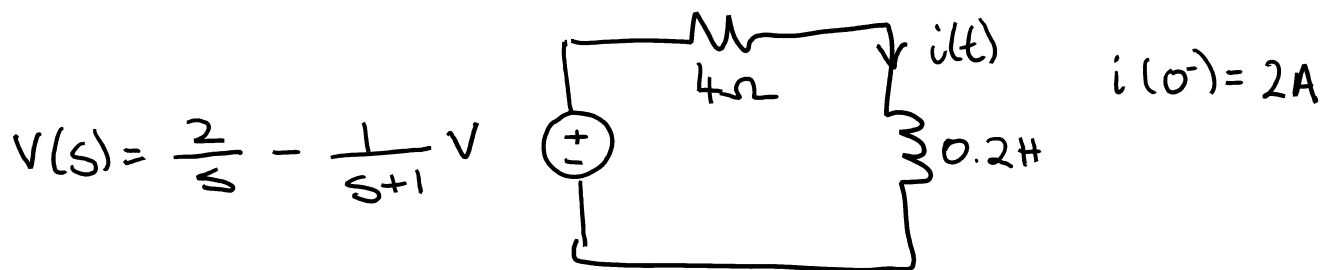For the circuit below, write the s-domain KVL equation in terms of $I(s)$. Rearrange and simplify the equation to get an s-domain expression for $I(s)$.



$$-\frac{2}{s} + \frac{1}{s+1} + 4I(s) + 0.2 \frac{dI(s)}{dt} = 0$$

$$4I(s) + 0.2 (sI(s) - i(0^-)) = \frac{2}{s} - \frac{1}{s+1}$$

$$4I(s) + 0.2sI(s) - 0.4 = \frac{2s+2-s}{s(s+1)}$$

$$I(s)(4 + 0.2s) = \frac{s+2}{s(s+1)} + 0.4$$

$$= \frac{s+2+0.4s^2+0.4s}{s(s+1)}$$

$$I(s) = \frac{0.4s^2 + 1.4s + 2}{s(s+1)(0.2s + 4)} \text{ A}$$

At Tutorial 8 – Unmarked Questions (9th August 2019)

Chapter 14, Ex 27: Laplace Transformations

Using the Laplace transform tables, determine $F(s)$ if $f(t)$ is equal to:

a) $3u(t-2)$

$$F(s) = \frac{3}{s} e^{-2s}$$

b) $3e^{-2} u(t) + 5u(t)$

$$\begin{aligned} F(s) &= \frac{3}{s+2} + \frac{5}{s} = \frac{3s + 5s + 10}{s(s+2)} \\ &= \frac{8s + 10}{s(s+2)} \end{aligned}$$

c) $\delta(t) + u(t) - tu(t)$

$$F(s) = 1 + \frac{1}{s} - \frac{1}{s^2} = \frac{s^2 + s - 1}{s^2}$$

d) $5\delta(t)$

$$F(s) = 5$$

Chapter 14, Ex 35: Laplace Transforms

Determine the inverse transform of $F(s)$ equal to:

a) $5 + \frac{5}{s^2} - \frac{5}{(s+1)}$

$$f(t) = 5\delta(t) + 5tu(t) - 5e^{-t}u(t)$$

b) $\frac{1}{s} + \frac{5}{0.1s+4} - 3$

$$F(s) = \frac{1}{s} + \frac{50}{s+40} - 3$$

$$f(t) = u(t) + 50e^{-40t}u(t) - 3\delta(t)$$

$$c) -\frac{1}{2s} + \frac{1}{(0.5s)^2} + \frac{4}{(s+5)(s+5)} + 2$$

$$F(s) = -\frac{1}{2s} + \frac{1}{0.25s^2} + \frac{4}{(s+5)^2} + 2$$


$$f(t) = -\frac{1}{2}u(t) + 4t u(t) + 4te^{-5t}u(t) + 2\delta(t)$$

$$d) \frac{4}{(s+5)(s+5)} + \frac{2}{s+1} + \frac{1}{s+3}$$

$$f(t) = 4te^{-5t}u(t) + 2e^{-t}u(t) + e^{-3t}u(t)$$

Chapter 14, Ex 46: Laplace Transformations

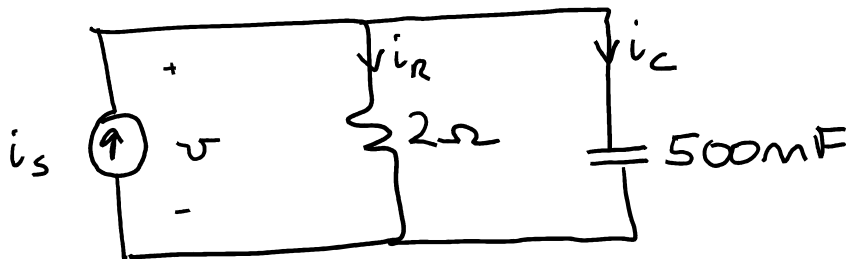For the circuit below, the initial voltage across the capacitor is $v(0^-) = 1.5$ V and the current source is $i_s = 700u(t)$ mA.



- a) Write the differential equation which arises from KCL, in terms of the nodal voltage $v(t)$.

$$i_s = i_R + i_C$$

$$0.7u(t) = \frac{v}{2} + 0.5 \frac{dv}{dt}$$

- b) Take the Laplace transform of the differential equation.

$$\frac{0.7}{s} = 0.5V(s) + 0.5(sV(s) - v(0^-))$$

$$= 0.5V(s) + 0.5sV(s) - 0.5 \times 1.5$$

$$0.7 = 0.5sV(s) - 0.5s^2V(s) - 0.75s$$

- c) Determine the frequency-domain representation of the nodal voltage

$$V(s)(0.5s^2 + 0.5s) = 0.7 + 0.75s$$

$$V(s) = \frac{0.7 + 0.75s}{s(0.5s + 0.5)}$$

Chapter 14, Ex 61: Impedance

The voltage $v(t) = 8e^{-2t}u(t)$ V is applied to a two-terminal device. Your assistant misunderstands you and only records the s -domain current which results. Determine what type of element it is and its value if $I(s)$ is equal to:

a) $\frac{1}{s+2}$ A

$$V(s) = \frac{8}{s+2}$$

$$\begin{aligned} Z(s) &= \frac{8/(s+2)}{1/(s+2)} \\ &= \frac{8}{s+2} \times \frac{s+2}{1} \\ &= 8\Omega \end{aligned}$$

\therefore an 8Ω resistor


b) $\frac{4}{s(s+2)}$ A

$$\begin{aligned} Z(s) &= \frac{8/(s+2)}{4/(s(s+2))} \\ &= \frac{8}{s+2} \times \frac{s(s+2)}{4} \\ &= \frac{8s}{4} \\ &= 2s\Omega \end{aligned}$$


\therefore a $2H$ inductor

Chapter 14, Ex 64a: Time-Domain Mesh Analysis, LT, Inverse LT

Referring to the circuit below and keeping the circuit in the time-domain, develop an expression for $i_c(s)$, then determine $i_c(t)$ for $t > 0$ if $i_s(t) = 2u(t+2)$ A and $v_s(t) = 2u(t)$ V. HINTS: You can work out the initial conditions using techniques from term 2. Use mesh analysis in the time domain for $t > 0$. Voltage drop across a capacitor is $v_c(t) = \frac{1}{C} \int_{t_0}^t i(T) dT + v_c(t_0)$.

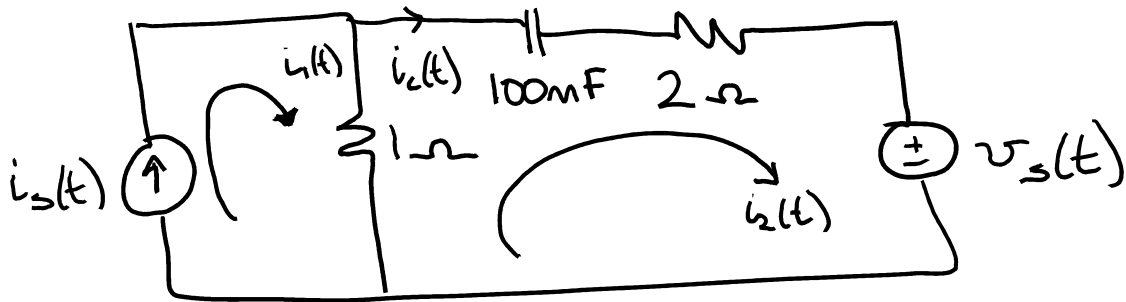

$t < 0$:

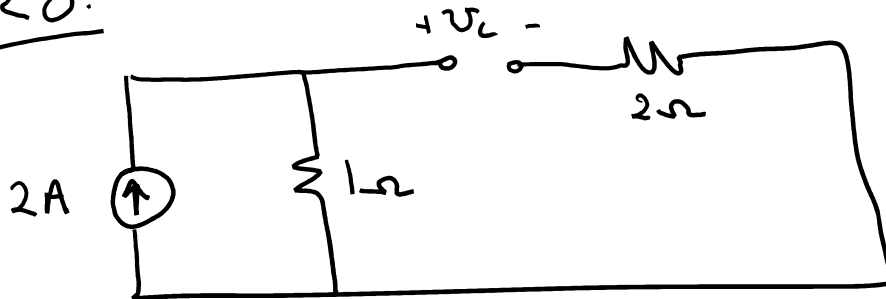

$$\begin{aligned} v_c(0^-) &= 2 \times 1 \\ &= 2V \\ &= v_c(0^+) \end{aligned}$$

$t > 0$:

mesh 2: $1(i_2 - i_1) + \frac{1}{0.1} \int_0^t i_2 dT + 2 + 2i_2 + 2 = 0$

$i_2 = i_c$ & $i_1 = 2$ by inspection

$$\therefore i_c - 2 + 10 \int_0^t i_c dT + 2i_c + 4 = 0$$

$$I_c(s) + \frac{10}{s} I_c(s) + 2I_c(s) = \frac{-2}{s}$$

$$I_c(s) \left(1 + \frac{10}{s} + 2 \right) = \frac{-2}{s}$$

$$I_c(s) \left(\frac{3s+10}{s} \right) = \frac{-2}{s}$$

$$I_c(s) = \frac{-2}{3s+10}$$

$$I_c(s) = -\frac{2}{3} \left(\frac{1}{s + 10/3} \right)$$

$$i_c(t) = -\frac{2}{3} e^{-10/3 t} u(t) \text{ A}$$