

Name:

Student ID:

Pre-tutorial 10 Questions (to be attempted before class on Sept 20th, 2019)

Chapter 16, Ex 2: Parallel RLC

A parallel RLC circuit is measured to have $Q_0 = 200$. Determine the missing component value (R, L or C) given the following component values:


a) $R = 1\ \Omega$ and $C = 1\ \mu\text{F}$.

b) $L = 12\ \text{fH}$ and $C = 2.4\ \text{nF}$.

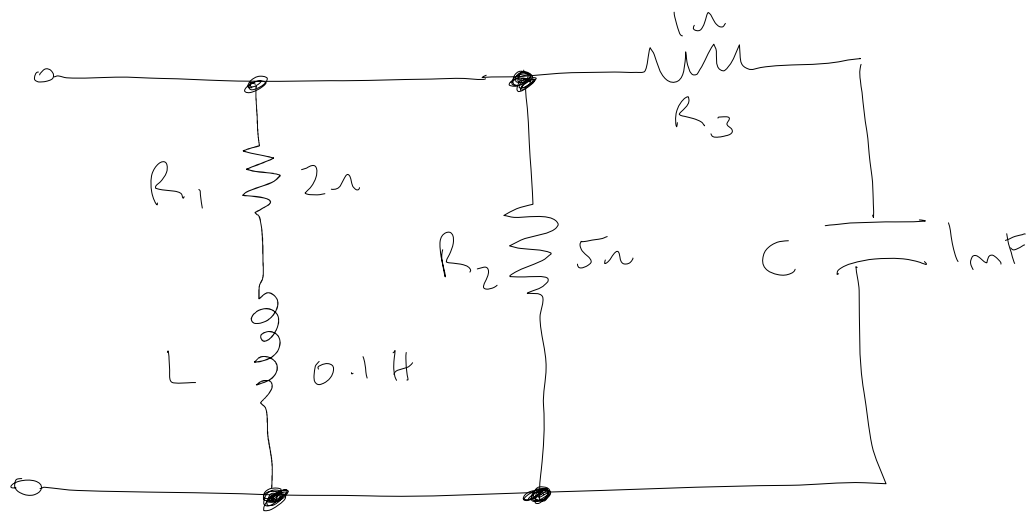c) $R = 121.7\ \text{k}\Omega$ and $L = 100\ \text{pH}$.

Chapter 16, Ex 6: Resonant frequency

Derive the resonant frequency of the network shown below. Keep in terms of R_1 , R_2 , R_3 , L and C (i.e. only substitute component values in once you have an equation for the resonant frequency).



NB:

$$j = \sqrt{-1}$$

$$j^2 = -1$$

$$-\frac{1}{j} = j$$