

Pre-tutorial 1 Questions

Chapter 2, Ex 26: Power

A fuse must be selected for a certain application. You may choose from fuses rated to “blow” when the current exceeds 1.5 A, 3 A, 4.5 A or 5 A. If the supply voltage is 110 V and the maximum allowed power dissipation is 500 W, which fuse should be chosen and why?

$$V = 110\text{V}$$

$$\text{Max power} = 500\text{W}$$

What is max current allowed?

$$P = VI \quad \text{or} \quad I_{\text{max}} = \frac{P_{\text{max}}}{V} = \frac{500}{110} = 4.545\text{A}$$

If choose fuse $I_{\text{max}} = 4.5\text{A}$

$$P = VI = 110 \times 4.5 = 495\text{W} \quad \checkmark$$


If choose fuse $I_{\text{max}} = 5\text{A}$

$$P = VI = 110 \times 5 = 550\text{W} \quad \times$$

Our choice is a little conservative. If device draws its maximum current of 500 W, then fuse blows.

Similar problem: ch 2 ex 27 in extra problems.

Chapter 3, Ex 38: KCL

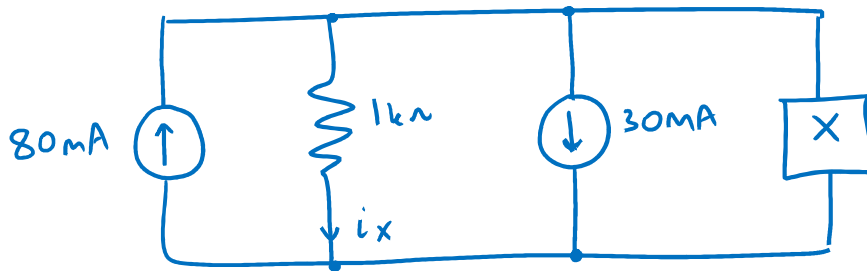


Using KCL, find the power absorbed by element X in the circuit above if it is a
(a) 4 kΩ resistor

$$\sum I_{in} = 0 \quad (\text{top node})$$

$$80\text{m} - \frac{V}{1\text{k}} - 30\text{m} - \frac{V}{4\text{k}} = 0$$

$$50\text{m} = \frac{5V}{4\text{k}}$$

$$V = 40\text{V}$$
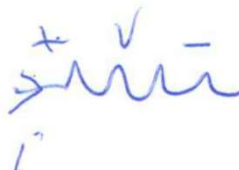
$$P = VI = \frac{V^2}{R} = \frac{40^2}{4\text{k}} = 400\text{mW} \text{ absorbed}$$


(b) 20mA independent current source (arrow down)

$$\sum I_{in} = 0$$


$$80\text{m} - \frac{V}{1\text{k}} - 30\text{m} - 20\text{m} = 0$$

$$30\text{m} = \frac{V}{1\text{k}}$$

$$V = 30\text{V}$$

$$P = VI = 30 \times 20\text{m} = 600\text{mW} \text{ absorbed}$$

(charging)

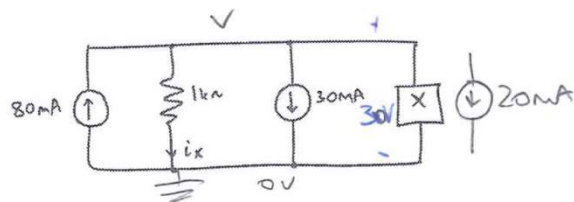

(c) dependent current source (arrow up, labelled $2i_x$)

$$\sum I_{in} = 0$$

$$80\text{mA} - i_x - 30\text{mA} + 2i_x = 0$$

$$i_x = -50\text{mA}$$

$$i_x = \frac{V}{1k}$$



$$\text{or } V = i_x \times 1k$$

$$= -50\text{V}$$

$$P = VI = -(-50) \times 2(-50\text{mA})$$

$$= \underline{\underline{-5\text{W}}}$$

absorbed
or 5W generated.

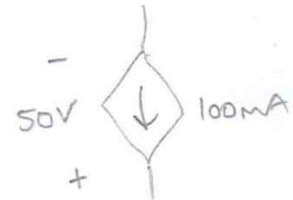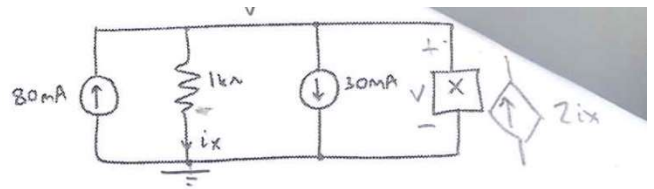

(d) 60V independent voltage source (+ at top)

$$i_x = \frac{V}{1k} = \frac{60}{1k} = 60\text{mA}$$


$$\sum I_{in} = 0$$

$$80\text{mA} - i_x - 30\text{mA} + i_s = 0$$

↑
60mA

$$i_s = 10\text{mA}$$
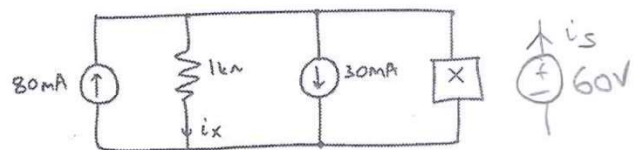
$$P = VI = 60(-10\text{mA}) = -600\text{mW}$$




You may want to try Ch 3 ex 36 with KCL.

At Tutorial 1 – Marked Question

Chapter 3, Ex 58: Equivalent resistance



Find the equivalent resistance, R_{eq} , for each of the three resistive networks shown.

a) Each resistor is $100\ \Omega$.

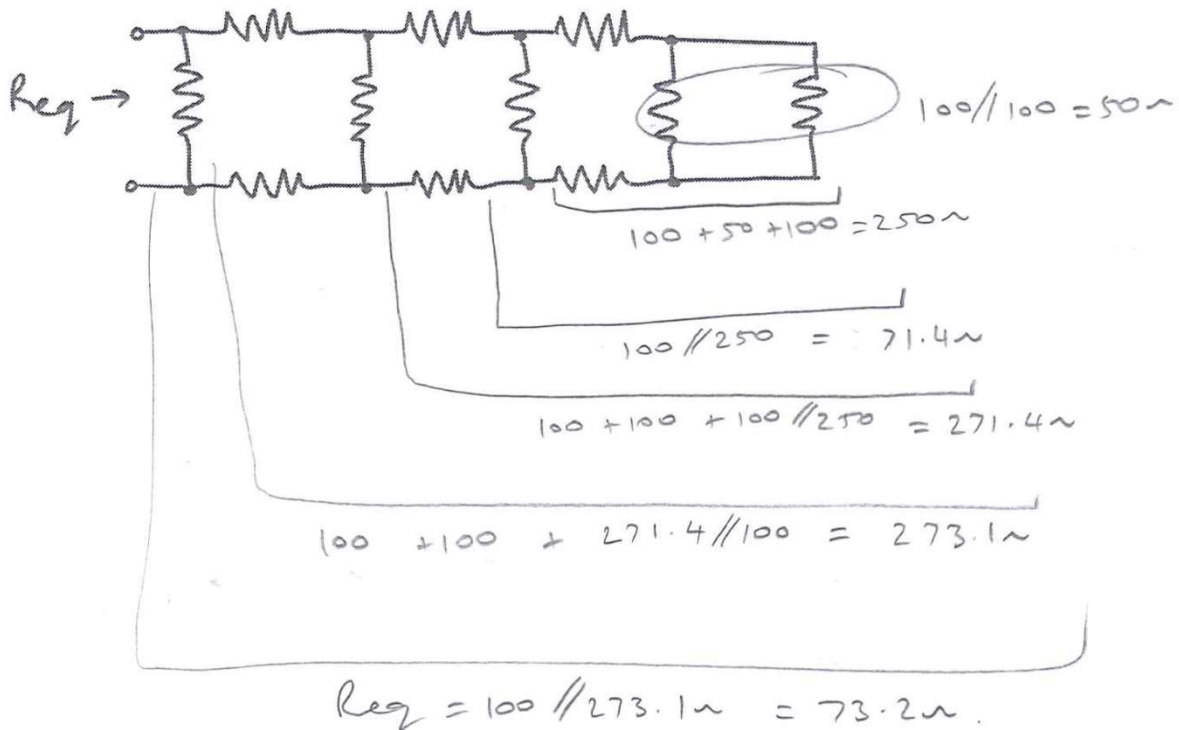

Chapter 3, Ex 58 cont.

b)

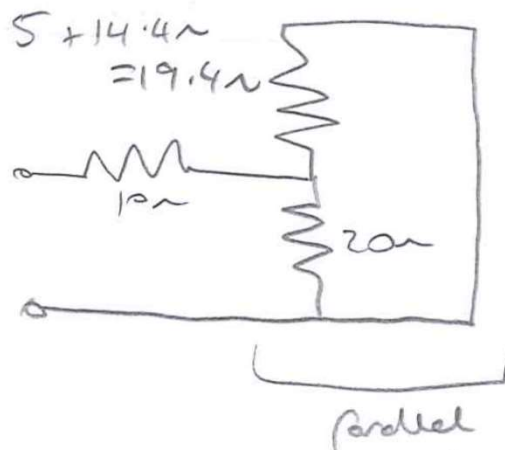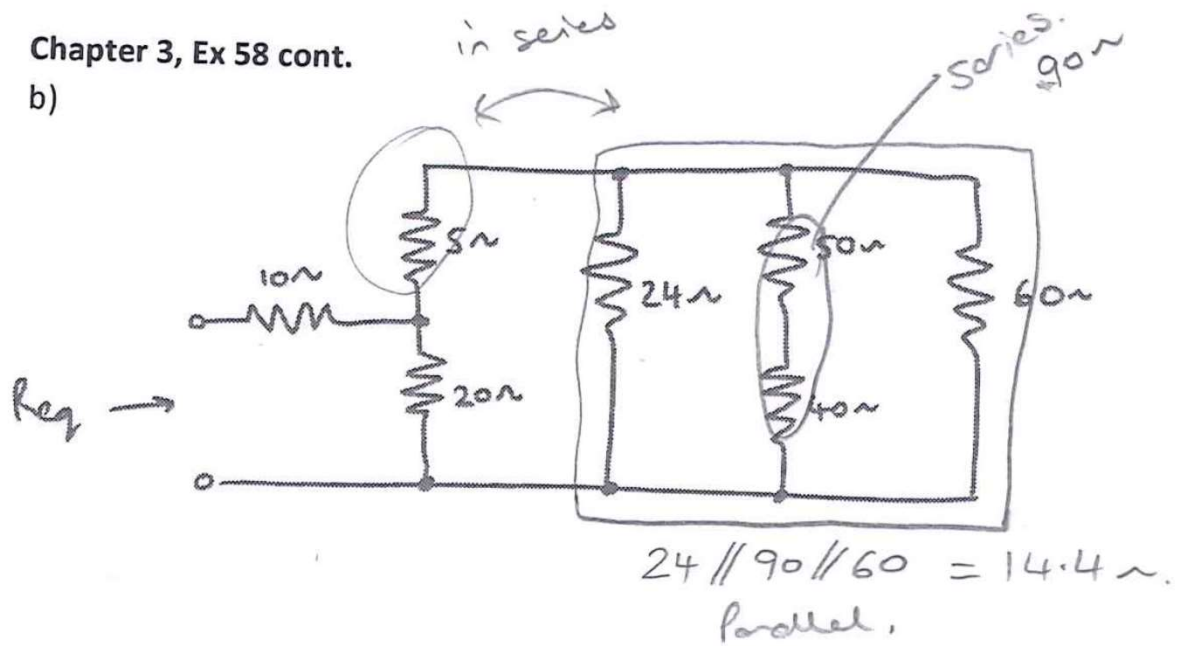



$$20 // 19.4\Omega = 9.85\Omega$$

$$R_{eq} = 10 + 9.85$$

$$= 19.85\Omega$$


Chapter 3, Ex 58 cont.

c)

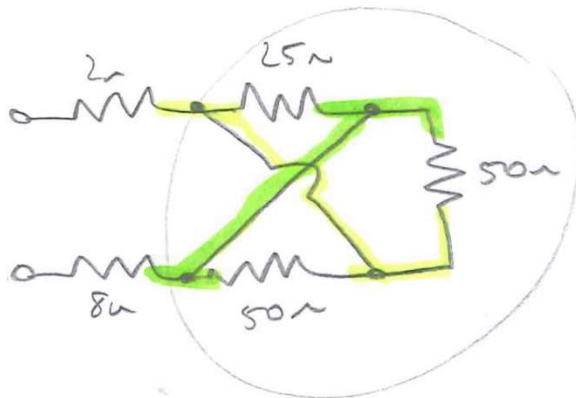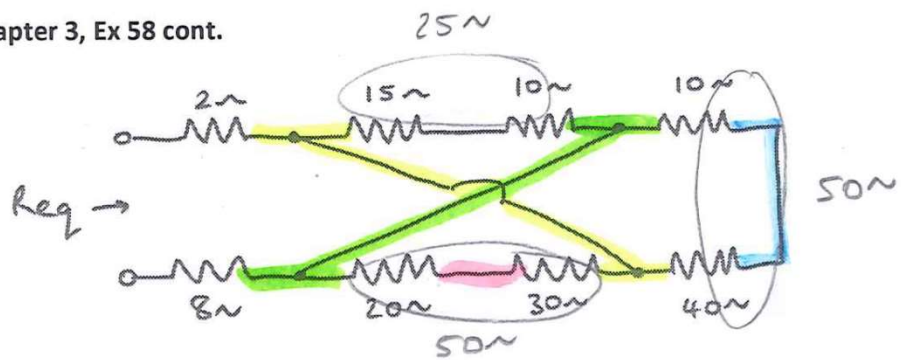

All 3 are between
green & yellow
nodes
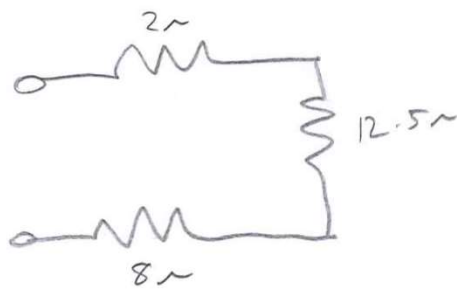
$$50 \parallel 25 \parallel 50 \\ = 12.5 \Omega$$



$$2 + 12.5 + 8 \\ = 22.5 \Omega$$

At Tutorial 1 – Unmarked Questions

Chapter 2, Ex 42: Ohm's Law

Determine the magnitude of the current flowing through a 4.7 kΩ resistor if the voltage across it is:

a) 1 mV

$$i = \frac{v}{R} = \frac{1 \times 10^{-3}}{4.7 \times 10^3} = 212.8 \text{ nA}$$

b) 10 V

$$i = \frac{10}{4.7 \times 10^3} = 2.13 \text{ mA}$$

c) $4e^{-t}$ V

$$i = \frac{4e^{-t}}{4.7 \times 10^3} = 851e^{-t} \mu\text{A}$$

d) $100 \cos(5t)$ V


$$i = \frac{100 \cos(5t)}{4.7 \times 10^3} = 21.3 \cos(5t) \text{ mA}$$

e) -7 V

$$i = \frac{-7}{4.7 \times 10^3} = -1.49 \text{ mA}$$

magnitude of $i = 1.49 \text{ mA}$

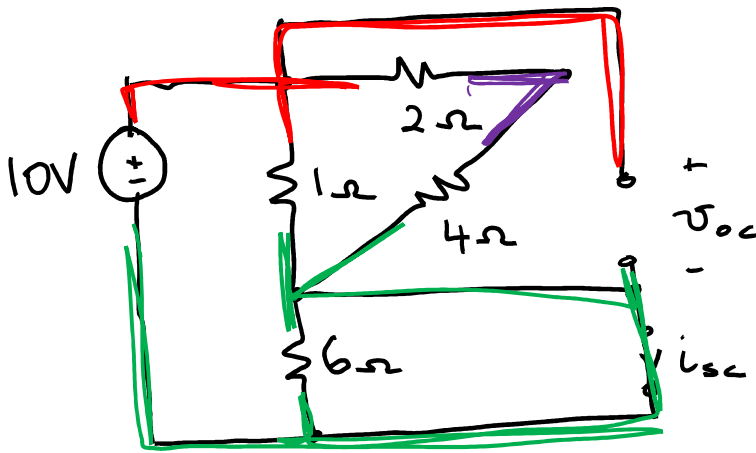KS Question 1: Parallel Components, Open Circuits, Short Circuits, Ohm's Law



For the circuit above, determine the following:

a) what (if anything) is in parallel

\Rightarrow voltage source, 1Ω resistor, and open circuit in \parallel




$\Rightarrow 6\Omega$ resistor & short circuit in \parallel
 $\therefore i_{6\Omega} = 0A$

b) the voltage across the open circuit

$$V_{oc} = V_{1\Omega} = V_S = 10V$$

c) the current through the short circuit


Redraw cot:

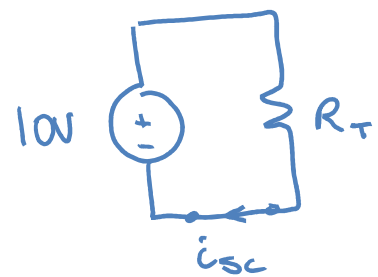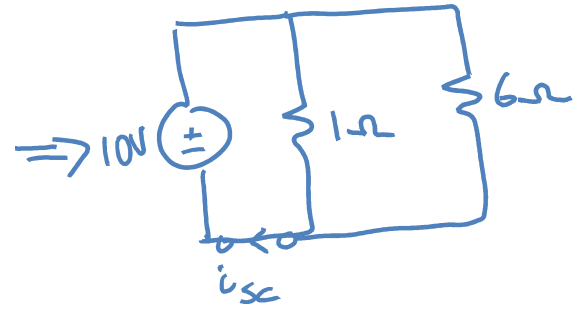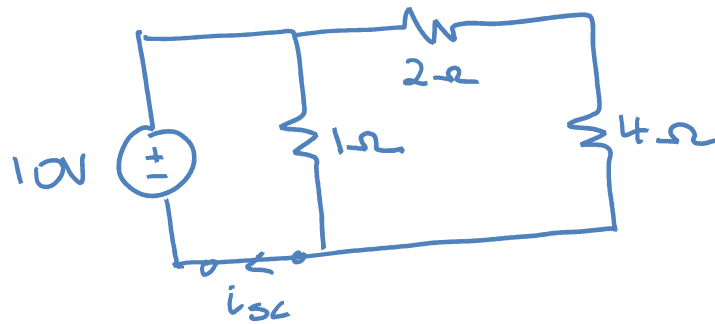

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$
$$= \frac{1 \times 6}{1 + 6} = \frac{6}{7} \Omega$$


$$i_{sc} = \frac{V}{R_T}$$
$$= \frac{10}{6/7} = 11.67 \text{ A}$$

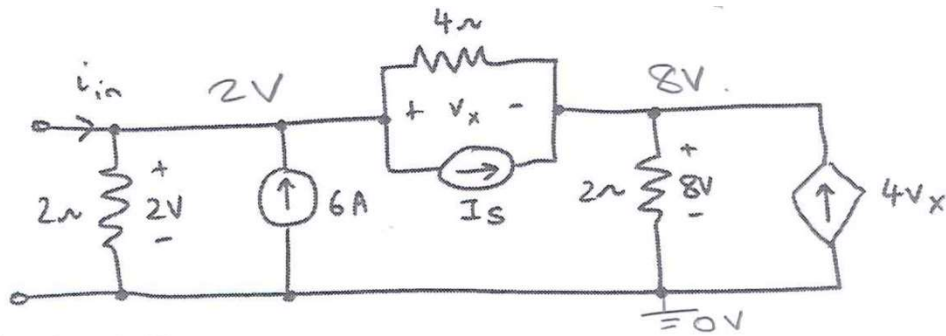Chapter 3 Ex 20: Ohm's and Kirchoff's laws



Use Ohm's and Kirchoff's laws on the circuit below to find

a) v_x

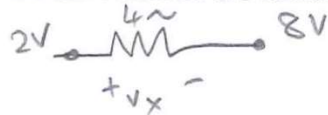

$$v_x = 2 - 8 = -6V.$$




b) I_s

$$\sum I_{in} = 0, KCL$$

$$I_s - 1.5 - 4 - 24 = 0$$

$$I_s = 29.5A$$

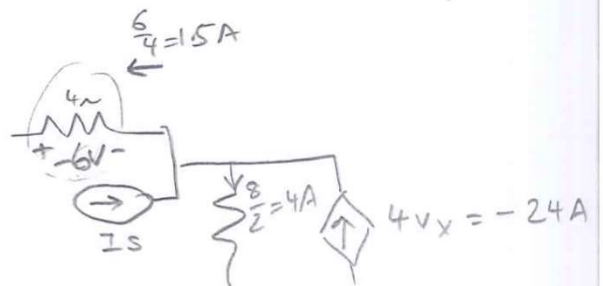


c) i_{in}


$$\sum I_{in} = \sum I_{out}$$

$$i_{in} + 6 + 1.5 = 1 + 29.5$$

$$i_{in} = 23A$$

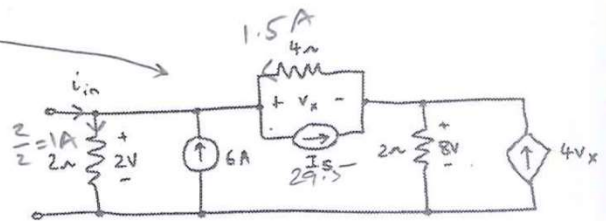

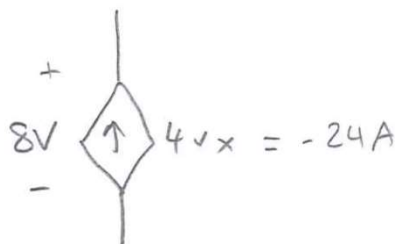d) the power supplied/ provided by the dependent source.




$$\begin{aligned} P_{supp} &= VI \\ &= 8 \times (-24) \\ &= -192W \end{aligned}$$

Extra Questions for Tutorial 1 (no worked solutions just final answer given)

Ch 2 ex 23 [Ans: $v_s = -1 \text{ mV}$]

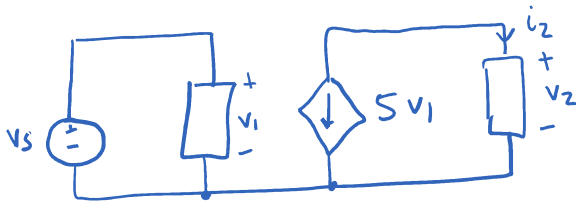For the circuit below, determine v_s if $v_2 = 1000i_2$ and $i_2 = 5 \text{ mA}$.



Ch 2, Ex 27 [Ans: a) $4.545 \text{ mA} - 5.556 \text{ mA}$. b) $22.73 \text{ mW} - 27.78 \text{ mW}$]

A $1 \text{ k}\Omega$ resistor with a 10% tolerance may have a value anywhere within the range $900 - 1100 \Omega$. Answer the following questions assuming 5.0 V is applied across the resistor.

- What is the range of currents that might be measured?
- What is the range of power that might be measured?

Ch 3 ex 36 [Ans: $i_x = 571.4 \mu\text{A}$]

Find the current i_x in the circuit below.

