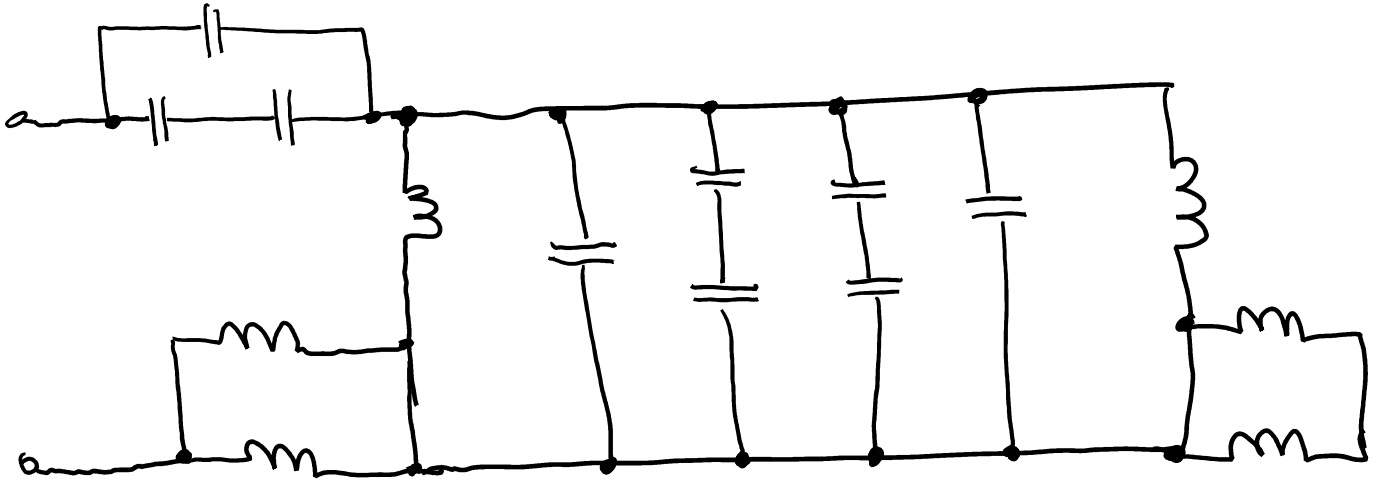


## At Tutorial 4 – Marked Question (3<sup>rd</sup> May 2019)

### Chapter 7, Ex 41: Equivalent capacitance/inductance


Reduce the network below to the smallest possible number of components if each inductor is 1 nH and each capacitor is 1 mF.



## At Tutorial 4 – Unmarked Questions (3<sup>rd</sup> May 2019)


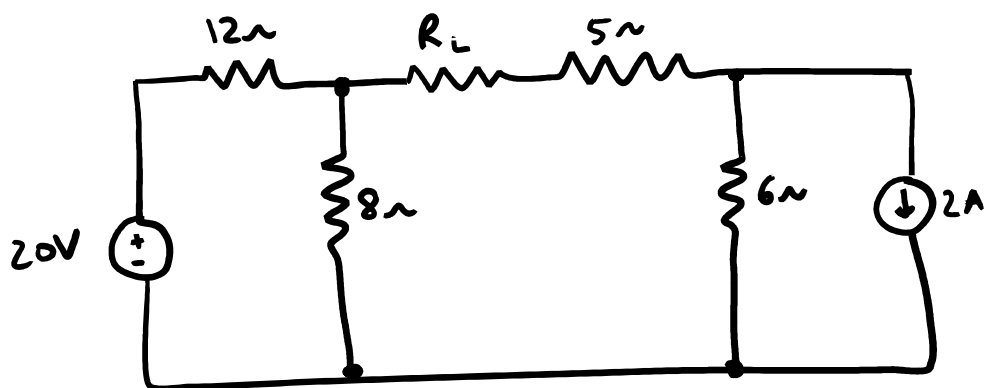
### Ch 5 ex 61: Maximum power transfer

Given you can select any value of  $R_L$ , what is the maximum power that could be delivered to  $R_L$ ?


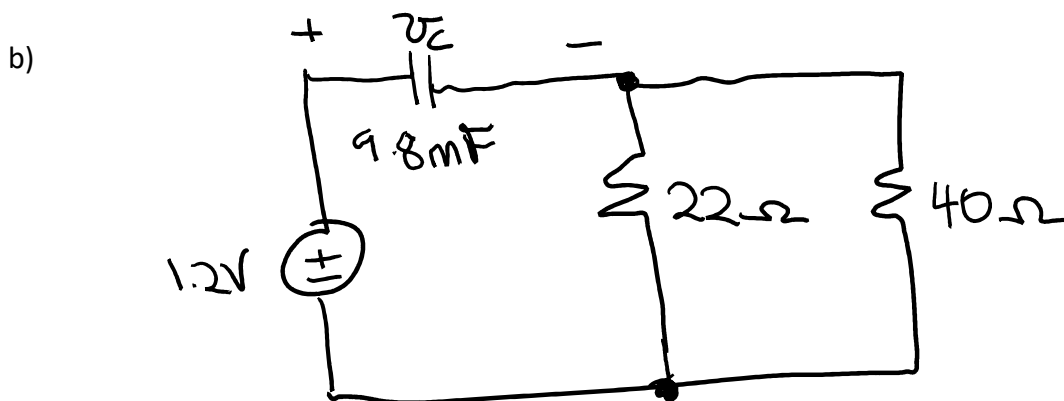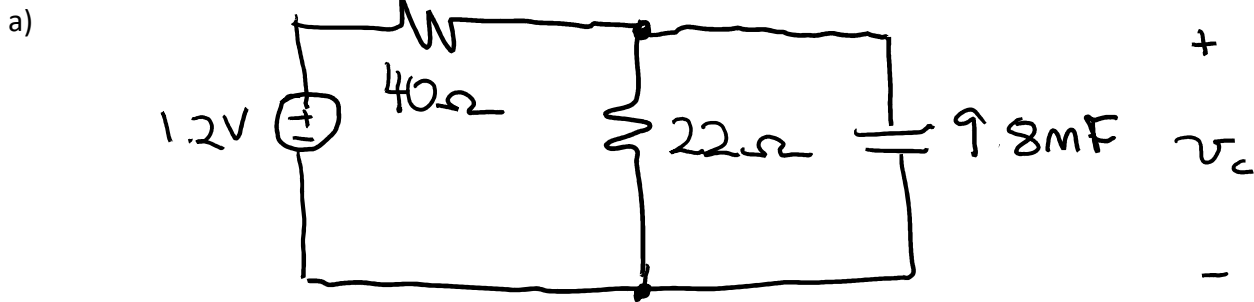
### Chapter 7, Ex 14: Power

Assume the circuits below have been connected for a long time. Calculate the power dissipated in the  $40\ \Omega$  resistor and the voltage labeled  $v_C$  in the circuits below:



### Chapter 7, Ex 27: Inductors

Determine the amount of energy stored in a  $33\text{ mH}$  inductor at  $t = 1\text{ ms}$  as a result of a current  $i_L$  given by:

- a)  $7\text{ A}$
- b)  $3 - 9e^{-1.3t}\text{ mA}$

### Chapter 7, Ex 25: Inductors

The voltage across a  $2\text{ H}$  inductor is given by  $v_L = 4.3t$ ,  $-0.1\text{ s} \leq t \leq 50\text{ ms}$ . Knowing that  $i_L(-0.1) = 100\ \mu\text{A}$ , calculate the current (assuming it is defined consistent with the passive sign convention) as  $t$  equal to:

- a)  $0$
- b)  $1.5\text{ ms}$
- c)  $45\text{ms}$