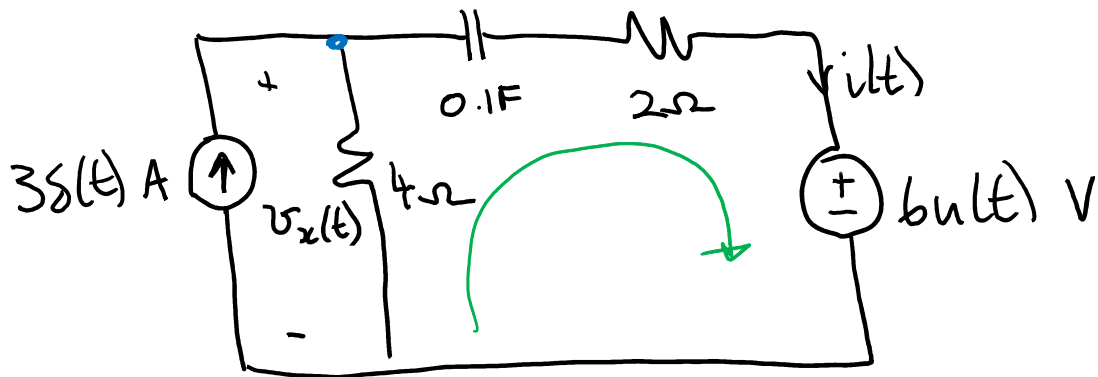


Example:

For the circuit below, write an equation with $i(t)$ as the only unknown. Take the LT, solve for $I(s)$, and then find $i(t)$ by taking the inverse LT. Assume the initial conditions are zero.



$$3\delta(t) = i(t) + \frac{v_x(t)}{4} \quad (\text{KCL} \Rightarrow \sum I_{in} = \sum I_{out})$$

$$v_x(t) = 12\delta(t) - 4i(t) \quad (1)$$

$$-v_x + \frac{1}{0.1} \int_{0^-}^{\infty} i(t) dt + 2i(t) + 6u(t) = 0 \quad (2) \quad (\text{KVL})$$

(1) into (2):

$$-12\delta(t) + 4i(t) + 10 \int_{0^-}^{\infty} i(t) dt + 2i(t) + 6u(t) = 0$$

$$-12 + 4I(s) + \frac{10}{s} I(s) + 2I(s) + \frac{6}{s} = 0$$

$$I(s) \left(6 + \frac{10}{s} \right) = 12 - \frac{6}{s}$$

$$I(s) = \frac{\frac{12s-6}{s}}{\frac{6s+10}{s}}$$

$$= \frac{12s-6}{6s+10}$$

$$= \frac{12s-6}{6(s+10/6)}$$

$$= \frac{A}{6} + \frac{B}{s+10/6}$$

$$= \frac{A(s+10/6) + 6B}{6(s+10/6)}$$

$$\therefore A(s + 10/6) + 6B = 12s - 6$$

$$\begin{aligned} \frac{s = -10/6}{6B} &= \frac{-120}{6} - 6 \\ &= -26 \\ B &= -4.33 \end{aligned}$$

$$\begin{aligned} As &= 12s \\ A &= 12 \end{aligned}$$

$$\begin{aligned} I(s) &= \frac{12}{6} - \frac{4.33}{s + 10/6} \\ &= 2 - \frac{4.33}{s + 1.67} \end{aligned}$$

$$i(t) = 2\delta(t) - 4.33e^{-1.67t}u(t) \quad A$$

$Z(s)$ and $Y(s)$

Readings: Section 14.7

Admittance and Impedance

Remember from the start of the term:

Impedance \Rightarrow voltage-current ratio

Admittance \Rightarrow current-voltage ratio

These definitions hold true in the s -domain too.

$$Z(s) = \frac{V(s)}{I(s)} \text{ and } Y(s) = \frac{I(s)}{V(s)} = \frac{1}{Z(s)}$$

Resistors

Very straightforward:

$$v(t) = i(t)R$$

$$V(s) = I(s)R$$

$$Z(s) = \frac{V(s)}{I(s)} = R \quad (\text{unit } \Omega)$$

$$Y(s) = \frac{I(s)}{V(s)} = \frac{1}{R} \quad (\text{unit } S)$$

Inductors

A little more complicated:

$$v(t) = L \frac{di}{dt}$$


$$V(s) = L(sI(s) - i(0^-))$$

If $i(0^-) = 0 \Rightarrow V(s) = LsI(s)$

$$\& \underline{Z(s) = sL} \quad (\Omega)$$

$$(\underline{i(0^-) = 0A})$$

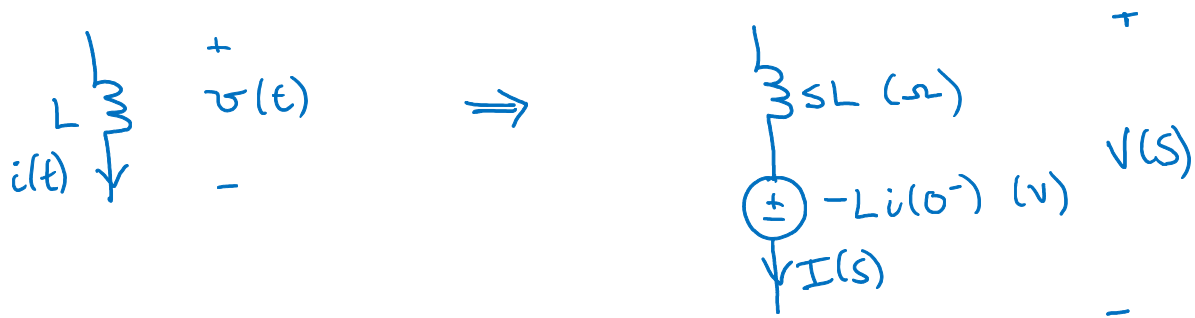We can now draw an inductor in the **s**-domain:




$\Rightarrow Li(0^-)$ will be a constant, which is why it can be modelled as a DC source.

Alternatively, if we want a current-based representation, we can rearrange our formula for **V(s)** to:

$$I(s) = \frac{V(s)}{sL} + \frac{i(0^-)}{s}$$

$$Y(s) = \frac{1}{sL} \text{ (s)}$$

$$Z(s) = sL \text{ (}\Omega\text{)}$$

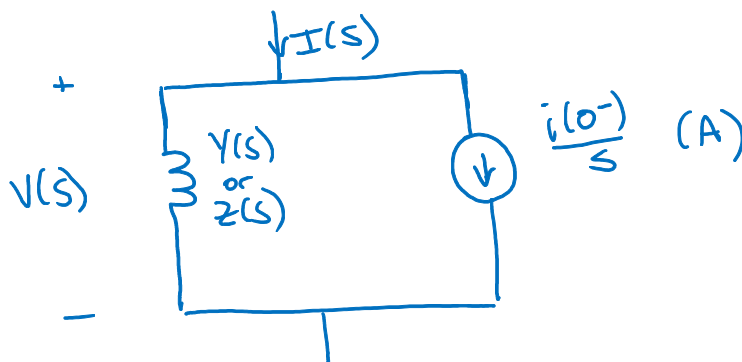

Capacitors

We can do a similar analysis for capacitors:

$$i(t) = C \frac{dv}{dt}$$


$$I(s) = C(sV(s) - v(0^-))$$

If $v(0^-) = 0 \Rightarrow I(s) = CsV(s)$

$$Z(s) = \frac{1}{sC} \text{ (}\Omega\text{)}$$

$$(v(0^-) = 0V)$$

Representing this as a circuit:

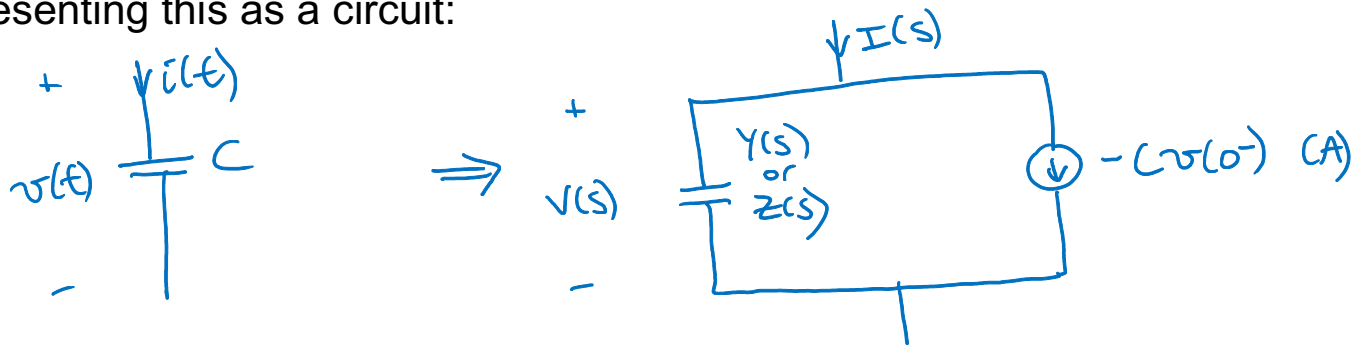

$$Y(s) = sC \text{ (S)}, \quad Z(s) = \frac{1}{sC} \text{ (}\Omega\text{)}$$

Again, $Cv(0^-)$ will be a constant, which is why we can represent it as a DC current source.

If we want a series representation, we can rearrange the equation to get:


$$\begin{aligned} V(s) &= \frac{I(s) + Cv(0^-)}{sC} \\ &= \frac{I(s)}{sC} + \frac{Cv(0^-)}{s} \end{aligned}$$

The diagram shows the series representation of the capacitor in the s-domain. It consists of an impedance $Z(s) = \frac{1}{sC}$ in series with a voltage source $\frac{Cv(0^-)}{s}$ (V). The total voltage is $V(s)$ and the current is $I(s)$.


We use these circuit representations to make analysis in the s -domain easier. Now we redraw the circuit in the s -domain and then analyse it, rather than taking the LT of everything after writing an expression in the time-domain.

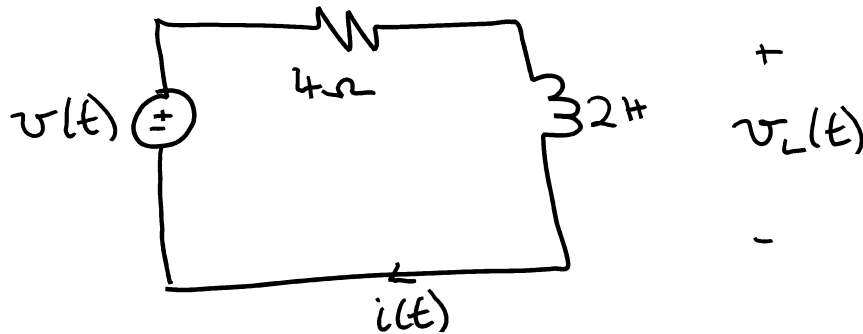Example

For the circuit below, find $v_L(t)$ if $v(t) = 6u(t)$ V, and $i(0^-) = 7$ A.



Redraw ckt in s-domain:

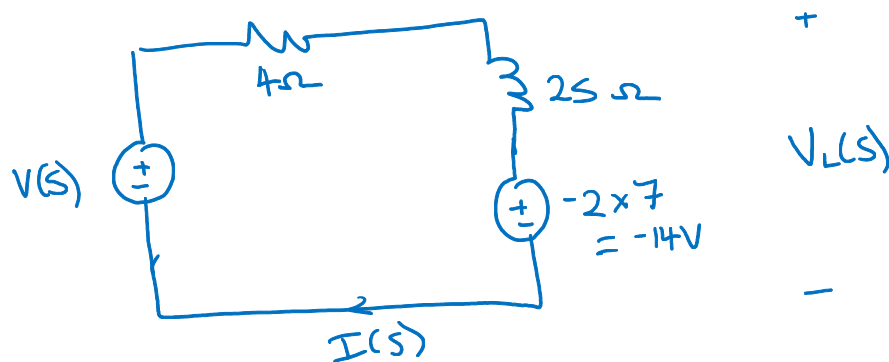

$$V(s) = \frac{6}{s} \text{ V}$$

$$-\frac{6}{s} + 4I(s) + 2sI(s) - 14 = 0 \quad (\text{KVL})$$

$$I(s)(4 + 2s) = 14 + \frac{6}{s}$$

$$I(s) = \frac{14s + 6}{s(4 + 2s)}$$

$$V_L(s) = 2sI(s) - 14$$


$$= 2s \left(\frac{14s + 6}{s(4 + 2s)} \right) - 14$$

$$= \frac{14s + 6}{2 + s} - 14$$

$$\begin{aligned}
 V_L(s) &= \frac{14s + 6 - 28 - 14s}{2 + s} \\
 &= \frac{-22}{s + 2} \\
 v_L(t) &= -22e^{-2t}u(t) \text{ V}
 \end{aligned}$$

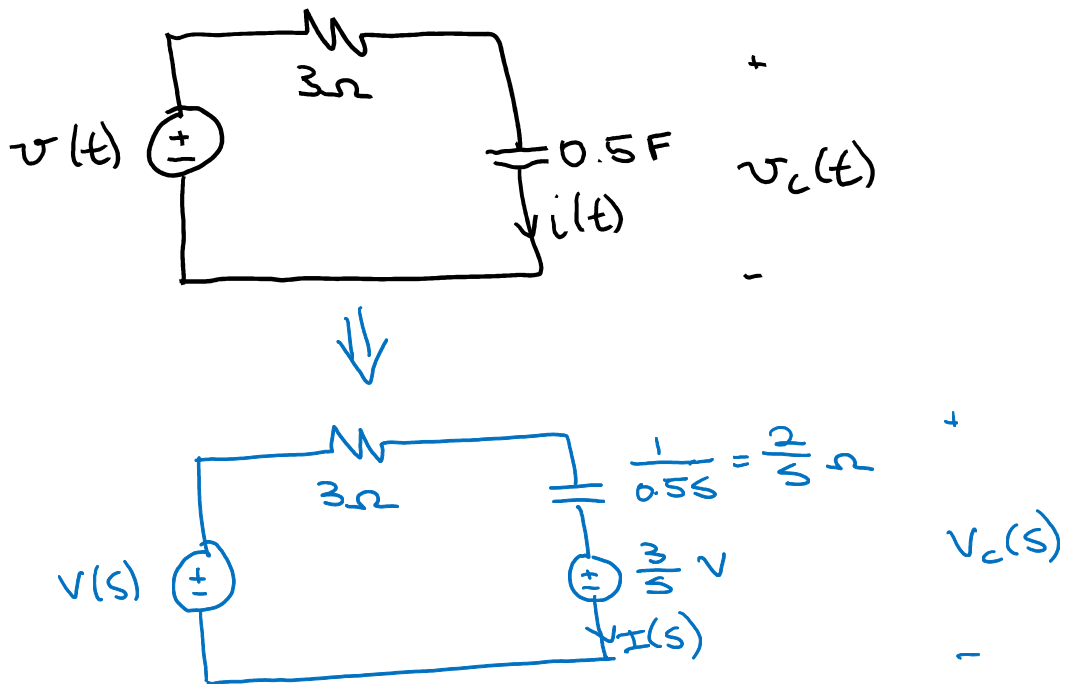Example

For the circuit below, what is $i(t)$ if $v(t) = 7e^{-3t}u(t)$ V and $v_c(0^-) = 3$ V?



$$V(s) = \frac{7}{s+3}$$

$$\frac{-7}{s+3} + 3I(s) + \frac{2}{s}I(s) + \frac{3}{s} = 0 \quad (\text{KVL})$$

$$I(s) \left(3 + \frac{2}{s} \right) = \frac{7}{s+3} - \frac{3}{s}$$

$$\left(\frac{3s+2}{s} \right) I(s) = \frac{7s-3s-9}{s(s+3)}$$

$$I(s) = \frac{s(4s-9)}{s(s+3)(3s+2)}$$

$$= \frac{4s-9}{(s+3)(3s+2)}$$

$$= \frac{3}{s+3} - \frac{5}{3s+2}$$

(need to do partial fractions)

$$i(t) = \left(3e^{-3t} - \frac{5}{3}e^{-2/3t} \right) u(t) \quad A$$