

Name:

Student ID:

### Pre-tutorial 3 Questions (to be attempted before class on March 29<sup>th</sup>, 2019)

#### Chapter 5, Ex 10: Superposition

Use superposition on the circuit below to find the voltage  $v$ . Note that there is a dependent source present.



