
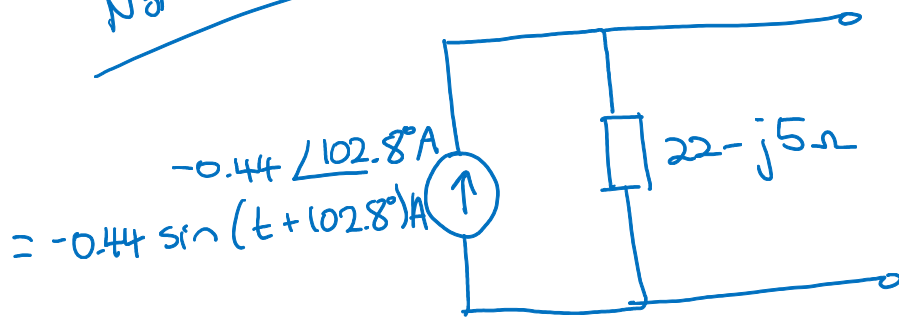


Norton Equiv.

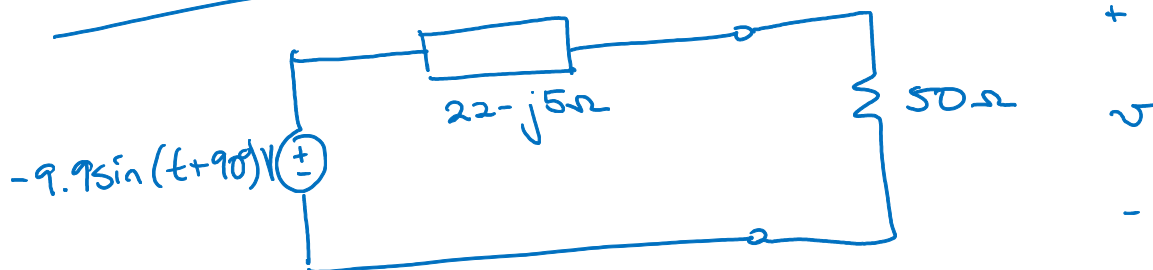

source transform:



$$\begin{aligned}\bar{V}_{Th} &= \bar{I} \bar{Z} \\ &= -0.44 \angle 102.8^\circ \times 22 - j5 \\ &= -0.44 \angle 102.8^\circ \times 22.56 \angle -12.8^\circ \\ &= -9.9 \angle 90^\circ \text{ V}\end{aligned}$$

$$\begin{aligned}\bar{V} &= \frac{50}{22 - j5 + 50} \times -9.9 \angle 90^\circ \\ &= \frac{-495 \angle 90^\circ}{72.17 \angle -3.97^\circ} \\ &= -6.86 \angle 93.97^\circ \text{ V}\end{aligned}$$

$$v(t) = -6.86 \sin(t + 93.97^\circ) \text{ V}$$



# Complex Frequency; Definition of the Laplace Transform

Readings: Sections 14.1, 14.2

## Complex Frequency

If we have a damped sinusoid for a source,  $x(t) = Ae^{\sigma t} \cos(\omega t + \phi)$ , then things get even more complicated. We can represent various types of waveforms, depending on the values of  $\sigma$  and  $\omega$ .

1.  $\sigma = \omega = 0$

$$x(t) = A \cos(\phi)$$

$\Rightarrow$  a constant i.e. DC

2.  $\sigma = 0$

$$x(t) = A \cos(\omega t + \phi)$$

$\Rightarrow$  a sinusoid

3.  $\omega = 0$

$$x(t) = Ae^{\sigma t} \cos(\phi)$$

$\Rightarrow$  an exponential

4. Neither equal 0

$$x(t) = Ae^{\sigma t} \cos(\omega t + \phi)$$

$\Rightarrow$  a damped sinusoid

Using Euler's formula, we can rearrange the general form to get:

$$x(t) = \operatorname{Re} \{ Ae^{(\sigma + j\omega)t + j\phi} \} = \operatorname{Re} \{ Ae^{j\phi} e^{st} \}$$

Complex frequency =  $s = \sigma + j\omega$


## The Laplace Transform

For a general function  $f(t)$ , the definition of the Laplace Transform is:

$$F(s) = \int_{-\infty}^{\infty} e^{-st} f(t) dt$$

As you can see from the limits of integration, this covers all of both positive and negative time. However, we're usually only interested in what happens after  $t = 0$  s, so we usually use the one-sided Laplace Transform instead:
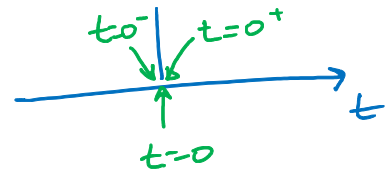
$$F(s) = \int_{0^-}^{\infty} e^{-st} f(t) dt$$



We use  $0^-$  rather than  $0$  or  $0^+$ , as we want to be able to use the initial conditions of the circuit.

Remember:

$$t(0^-) \neq t(0) \neq t(0^+)$$

$\therefore v(0^-), v(0), v(0^+)$  could all be different,  
as can  $i(0^-), i(0), i(0^+)$

Voltage across a capacitor,  $v_C$ , and current through an inductor,  $i_L$ , are special cases. Other voltages and currents can change instantly.

Notation (hand-written):

$$\mathcal{L}[f(t)] = F(s)$$

Notation (typed):


$$\mathcal{L}[f(t)] = \mathbf{F(s)}$$

**Example:**

Work out the LT of  $f(t) = 3u(t - 6)$  using the LT formula.

$$\begin{aligned} F(s) &= \int_{0^-}^{\infty} e^{-st} f(t) dt \\ &= \int_{0^-}^{\infty} e^{-st} \times 3u(t-6) dt \end{aligned}$$

$u(t-6)$  looks like:

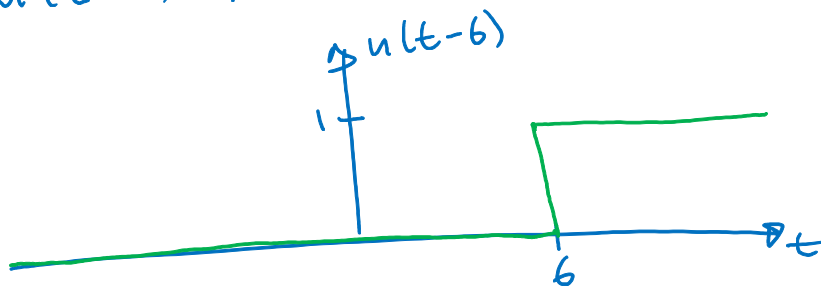

$$\begin{aligned} \therefore F(s) &= 3 \int_6^{\infty} e^{-st} dt \\ &= 3 \left[ -\frac{1}{s} e^{-st} \right]_6^{\infty} \\ &= 3 \left[ 0 - \left( -\frac{1}{s} e^{-6s} \right) \right] \\ &= \frac{3}{s} e^{-6s} \end{aligned}$$

**Example:**

What is the one-sided LT of  $f(t) = e^{-3t}$ ?


$$\begin{aligned} F(s) &= \int_{0^-}^{\infty} e^{-st} e^{-3t} dt \\ &= \left[ \frac{-1}{s+3} e^{-(s+3)t} \right]_{0^-}^{\infty} \\ &= 0 - \left( -\frac{1}{s+3} \right) \\ &= \frac{1}{s+3} \end{aligned}$$

# Laplace transforms of simple time functions; Basic theorems for the Laplace transform


Readings: Sections 14.3, 14.5
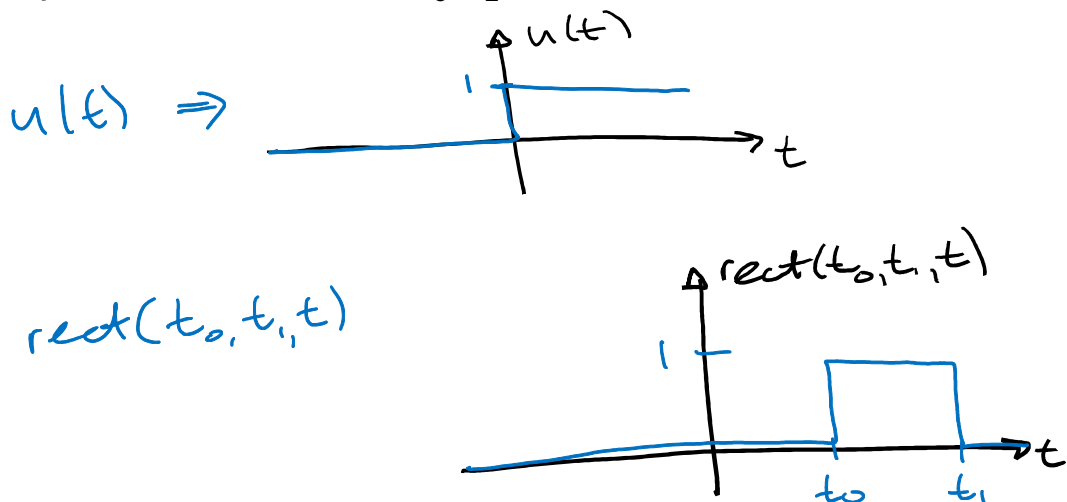
## More Useful Functions


Reminder: in Term 2 we looked at the unit step function,  $u(t)$ , and the rectangular pulse function,  $\text{rect}(t_0, t_1, t)$ :



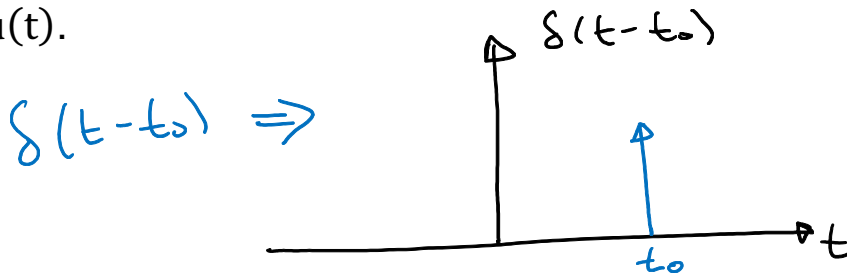We will add to that the unit impulse,  $\delta(t - t_0)$ , and the ramp function,  $tu(t)$ .



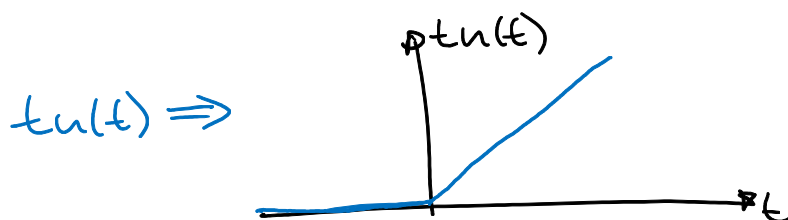The unit impulse has *infinite* amplitude at one instant in time. The area “under” the unit impulse is defined as equal to 1. A really useful function.



The unit ramp has zero amplitude for  $t < 0$  s, but is equal to  $t$  for positive time.

## Properties of the Laplace transform

To be able to use the LT on a circuit, we need to know a few more things... Equations for circuits with capacitors and inductors in them usually look something like this (assuming initial conditions are zero):

$$v(t) = Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int i(t) dt$$

So – can we add LTs? How do we deal with differentials and integrals?

1. Linearity: Since the LT is calculated using integration, and we know that  $\int (a + b) = \int a + \int b$ , then it makes sense that:

$$\begin{aligned} \mathcal{L}[f_1(t) + f_2(t)] &= \mathcal{L}[f_1(t)] + \mathcal{L}[f_2(t)] \\ &= F_1(s) + F_2(s) \end{aligned}$$

Similarly, if  $b$  is a constant, then:

$$\begin{aligned} \mathcal{L}[bf(t)] &= b \mathcal{L}[f(t)] \\ &= b F(s) \end{aligned}$$

2. Differentiation and Integration in the Time Domain: Using integration by parts you can show that:


$$\begin{aligned} \mathcal{L}\left[\frac{d^1 f}{dt}\right] &= sF(s) - f(0^-) \\ \mathcal{L}\left[\frac{d^2 f}{dt^2}\right] &= s^2 F(s) - sf(0^-) - f'(0^-) \\ \mathcal{L}\left[\int_0^t f(x) dx\right] &= \frac{1}{s} F(s) \end{aligned}$$

3. Time Shift: This helps us deal with situations where we might have different switches turning on at different points in time.

$$\begin{aligned}
 \mathcal{L}[f(t-a)u(t-a)] &= \int_{0^-}^{\infty} e^{-st} f(t-a) u(t-a) dt \\
 &= \int_{a^-}^{\infty} e^{-st} f(t-a) dt \\
 &\quad \text{set } \tau = t-a \\
 &= \int_{0^-}^{\infty} e^{-s(\tau+a)} f(\tau) d\tau \\
 &= e^{-as} \int_{0^-}^{\infty} e^{-s\tau} f(\tau) d\tau \\
 &= e^{-as} F(s)
 \end{aligned}$$
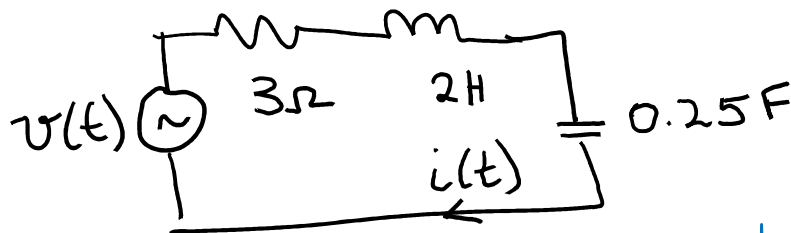
### Example:

For the circuit below, find  $\mathbf{I(s)}$  in terms of  $\mathbf{V(s)}$  if  $i(0^-) = 0$  A.



$$v(t) = 3i(t) + 2 \frac{di}{dt} + 4 \int_0^t i(\tau) d\tau$$

$$V(s) = 3I(s) + 2(sI(s) - \cancel{i(0^-)}) + \frac{4}{s} I(s)$$

$$= 3I(s) + 2sI(s) + \frac{4}{s} I(s)$$

$$I(s) = \frac{V(s)}{3 + 2s + 4/s}$$



$$I(s) = \frac{sV(s)}{3s + 2s^2 + 4}$$

What does  $I(s)$  look like if  $v(t) = u(t)$ ?

$$\begin{aligned} V(s) &= \int_0^{\infty} e^{-st} u(t) dt \\ &= \int_0^{\infty} e^{-st} dt \\ &= \frac{1}{s} \end{aligned}$$

$$\begin{aligned} I(s) &= \frac{s(1/s)}{2s^2 + 3s + 4} \\ &= \frac{1}{2s^2 + 3s + 4} \end{aligned}$$

We can use tables of LT pairs rather than integrating – this is normally faster and easier. The tables are at the start of this book, and are the same ones you will get in the exam.

### General Process

1. Write an equation for  $i(t)$  and/or  $v(t)$ .
2. Take the Laplace Transform and get  $I(s)$  and/or  $V(s)$
3. Rearrange the equation(s) as desired
4. Take the inverse LT to get back into the time domain (see next section)