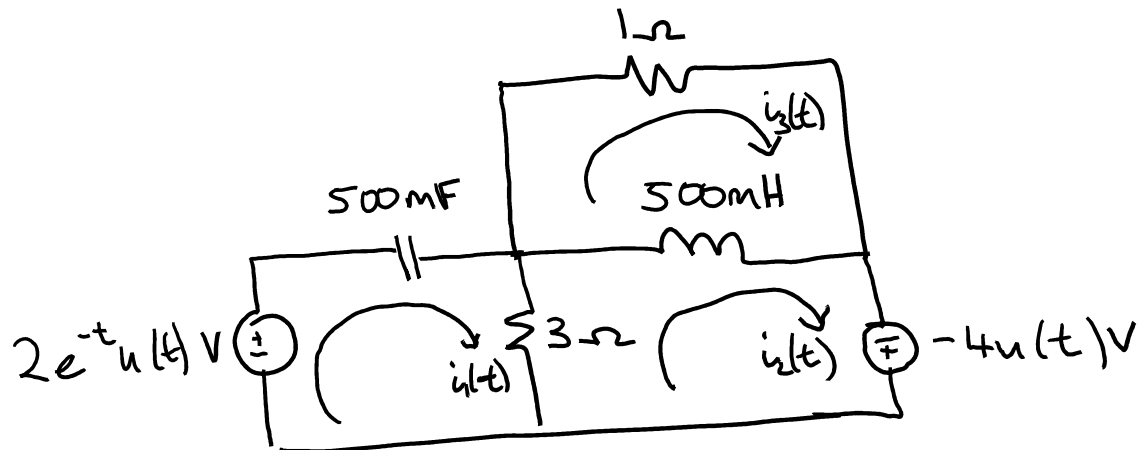


Name:

Student ID:

Pre-tutorial 9 Questions (to be attempted before class on August 23rd, 2019)

Chapter 15, Ex 11: s-Domain Mesh Analysis



For the circuit drawn above:

a) Draw the s-domain equivalent. Hint: You can work out the initial conditions by inspection.

b) Write the three s-domain mesh equations, and simplify so they are in the form $aI_1(s) + bI_2(s) + cI_3(s) = d$.

Chapter 15, Ex 31: Poles and Zeros

Determine the poles and zeros for the following s-domain functions:

a) $\frac{s}{s+12.5}$

b) $\frac{s(s+1)}{(s+5)(s+3)}$

c) $\frac{s+4}{s^2+8s+7}$

d) $\frac{s^2-s-2}{3s^3+24s^2+21s}$