
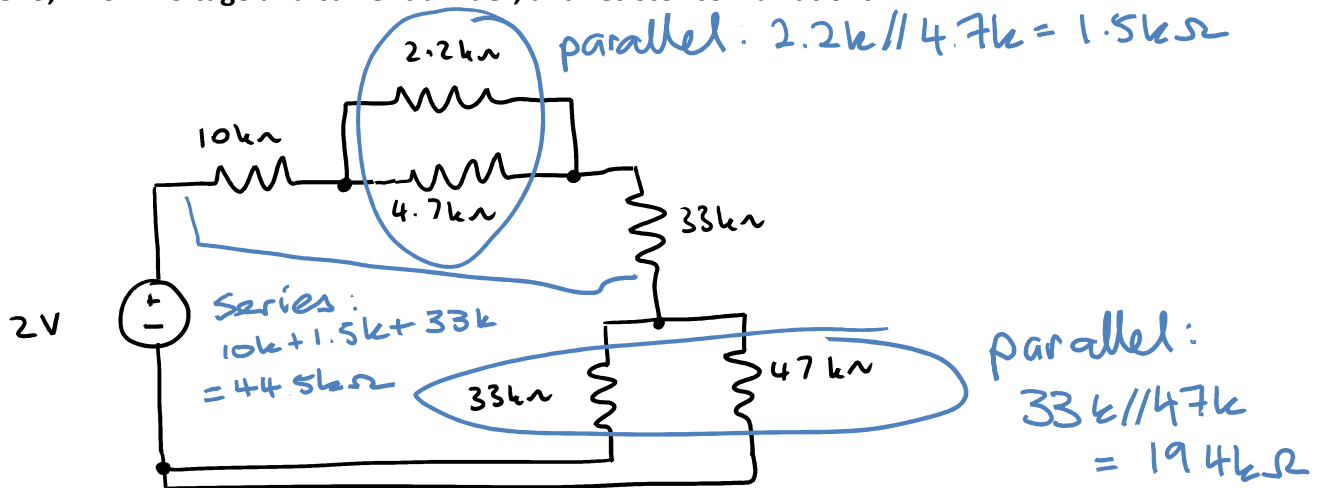


Pre-tutorial 2 Questions

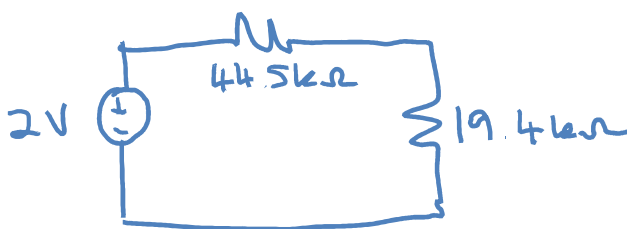Chapter 3, Ex 67: Voltage and current divider, and resistor combinations




- a) Use voltage division to calculate the voltage across the 47 kΩ resistor in the circuit above.




$$V_{47k} = 2 \times \frac{19.4k}{19.4k + 44.5k} = 607mV$$

- b) Find the current down the 47 kΩ resistor using current divider.

Current through main loop:

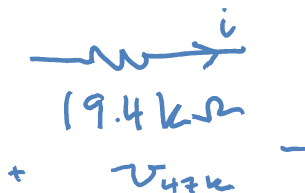

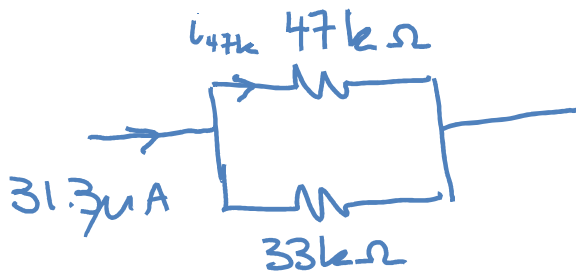
$$i = \frac{V}{R} = \frac{607 \times 10^{-3}}{19.4 \times 10^3} = 31.3\mu A$$



$$i_{47k} = \frac{31.3\mu \times 33k}{47k + 33k} = 12.9\mu A$$

Chapter 4, Ex 19: Nodal analysis

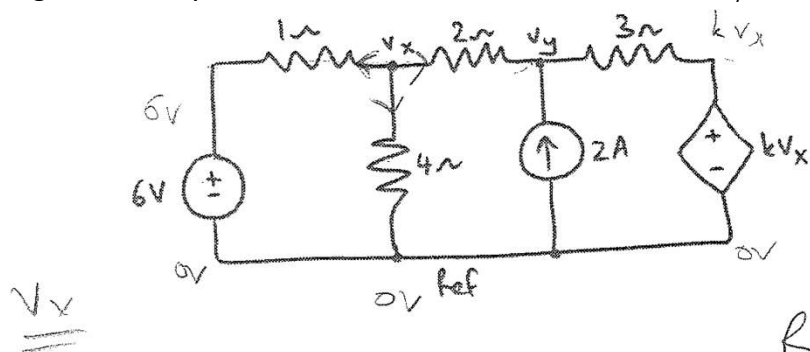Using nodal analysis, find the value of k that will result in $v_y = 0$ in the circuit below.



$$\sum I_{out} = 0$$

$$\frac{v_x - 6}{1} + \frac{v_x}{4} + \frac{v_x - v_y}{2} = 0$$

$$7v_x - 2v_y = 24 \quad \xrightarrow{v_y=0} \quad 7v_x = 24 \quad (1)$$



$$\sum I_{out} = 0$$

$$\frac{v_y - v_x}{2} - 2 + \frac{v_y - kv_x}{3} = 0 \quad (2)$$

$$5v_y - v_x(3 + 2k) = 12 \quad \xrightarrow{v_y=0} \quad -3v_x - 2kv_x = 12$$

From (1)

$$v_x = 24/7 = 3.429V$$

From (2)


$$k = \frac{-12 - 3v_x}{2v_x} = -3.250$$

At Tutorial 2 – Marked Question

Chapter 5, Ex 45: Thévenin equivalent (use nodal analysis)

For the network below:

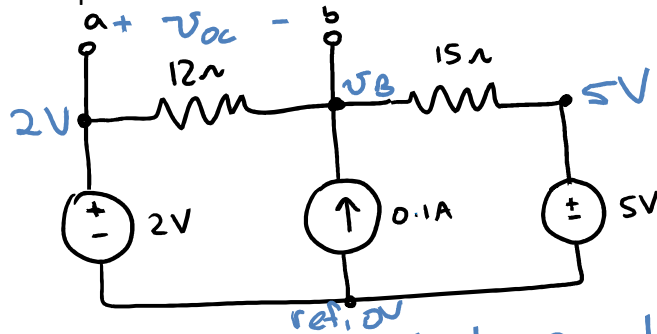a) find the Thévenin equivalent seen at terminals a and b.



Find v_{oc} using nodal analysis

$$\sum I_{out} = 0 \text{ at node B}$$

$$\frac{v_B - 2}{12} - 0.1 + \frac{v_B - 5}{15} = 0$$

$$\frac{5v_B - 10 + 4v_B - 20}{60} = 0.1$$


$$9v_B - 30 = 6$$

$$9v_B = 36$$

$$v_B = 4V$$


$$v_{oc} = 2 - v_B = -2V$$

R_{TH}

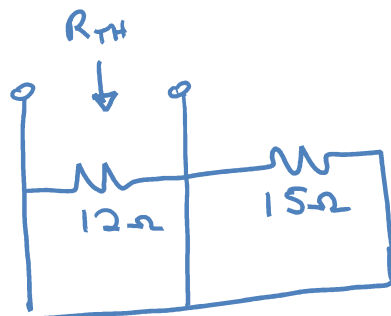


$$R_{TH} = 12 \parallel 15 = 6.67\Omega$$


Thévenin ckt:

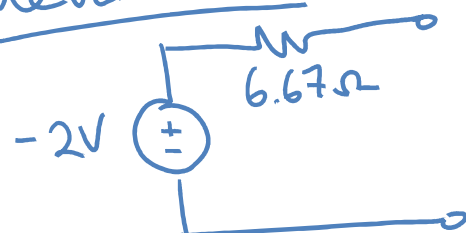

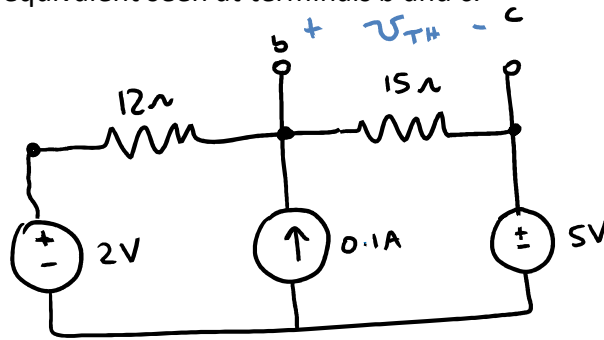b) find the Thévenin equivalent seen at terminals b and c.





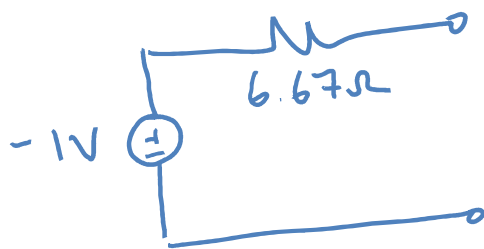$\Rightarrow V_B$ is the same as before. $\therefore V_B = 4V$
 $V_{TH} = 4 - 5 = -1V$
 $R_{TH} = 15 \parallel 12 = 6.67\Omega$



Thévenin ckt

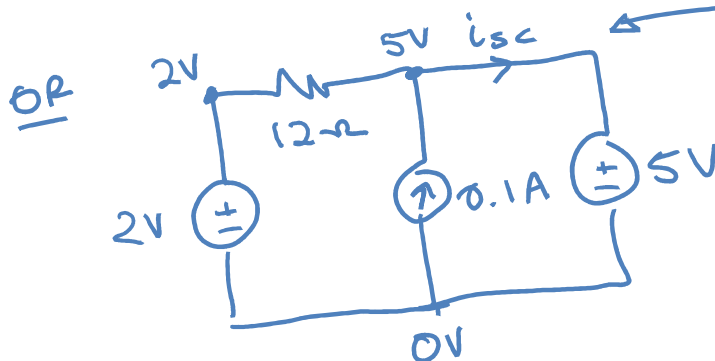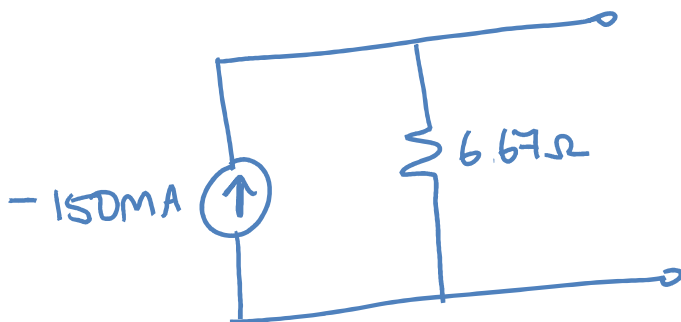Norton
 $i_N = \frac{V_{TH}}{R_{TH}} = -150mA$



SC in \parallel w 15Ω resistor, so can remove $R_{15\Omega}$.


$$i_{sc} = 0.1 + \frac{2-5}{12}$$

$= 150mA$ as before \checkmark

At Tutorial 2 – Unmarked Questions

Chapter 4, Ex 16: Nodal analysis

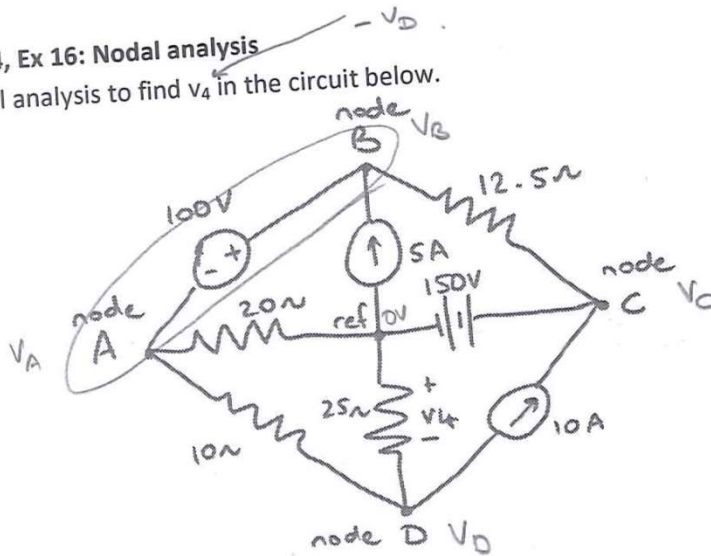Use nodal analysis to find v_4 in the circuit below.



Supernode A-B : $\sum I_{out} = 0$

$$\frac{V_A}{20} + \frac{V_A - V_D}{10} + \frac{V_B - V_C}{12.5} - 5 = 0$$

$$0.15V_A + 0.08V_B - 0.08V_C - 0.1V_D = 5 \quad (1)$$

Extra equation $V_B - V_A = 100 \quad (2)$

Node C

By observation $V_C = 150V$

Node D $\sum I_{out} = 0$

$$\frac{V_D - V_A}{10} + \frac{V_D}{25} + 10 = 0$$

$$-25V_A + 35V_D = -2500 \quad (3)$$

↓


$$V_D = -63.06V$$

But $V_D = -v_4$

$$\Rightarrow v_4 = 63.06V$$

Chapter 5, Ex 63: Thévenin equivalent

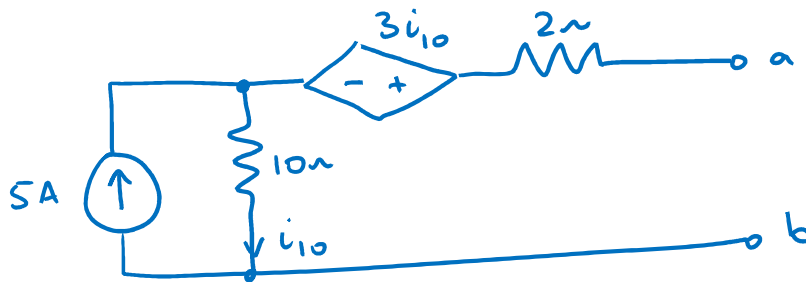
a) Determine the Thévenin equivalent of the network shown below.



V_{oc}

$$i_{10} = 5A \quad \text{by inspection}$$
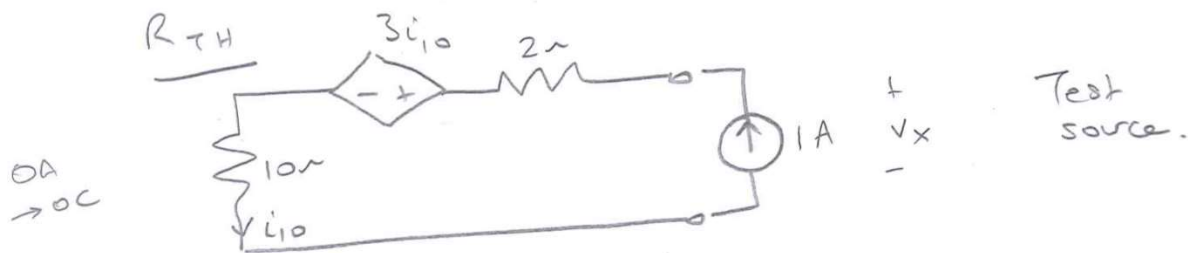
$$\begin{aligned} V_{TH} &= 10i_{10} + 3i_{10} \\ &= 13 \times 5 \\ &= 65V \end{aligned}$$




$$V_x = 2 \times 1 + 3i_{10} + 10i_{10} \quad (\text{KVL})$$

$$i_{10} = 1A$$

$$\rightarrow V_x = 15V$$

$$R_{TH} = \frac{V_x}{1} = 15\Omega$$

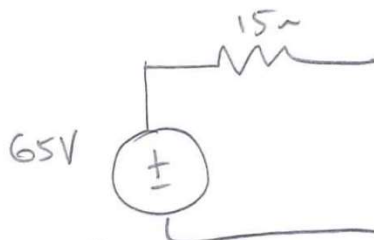
or could calculate i_{sc} and use ohms law.



Extra Questions for Tutorial 2 (no worked solutions just final answer given)


Ch 3, Ex 74: Current divider [Ans: $i_x = 2.837$ A, $i_y = 2.853$ A, $P = 51.59$ W]

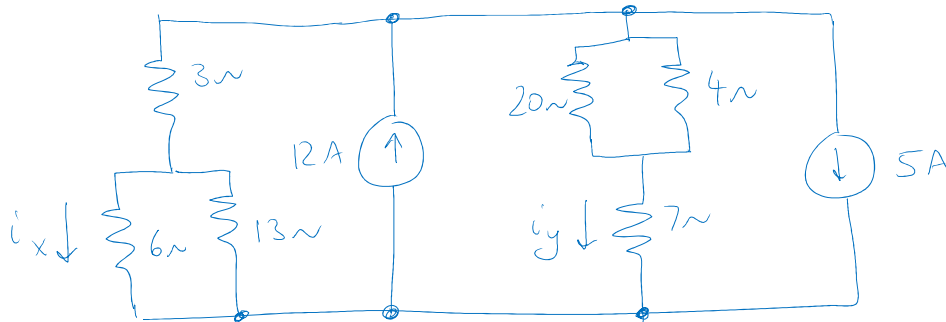For the circuit below, find i_x , i_y and the power dissipated/ absorbed by the $3\ \Omega$ resistor.




Ch 4, Ex 9: Nodal analysis [Ans: $v_1 = 58.5$ V, $v_2 = 64.4$ V, $P = 543.4$ W]

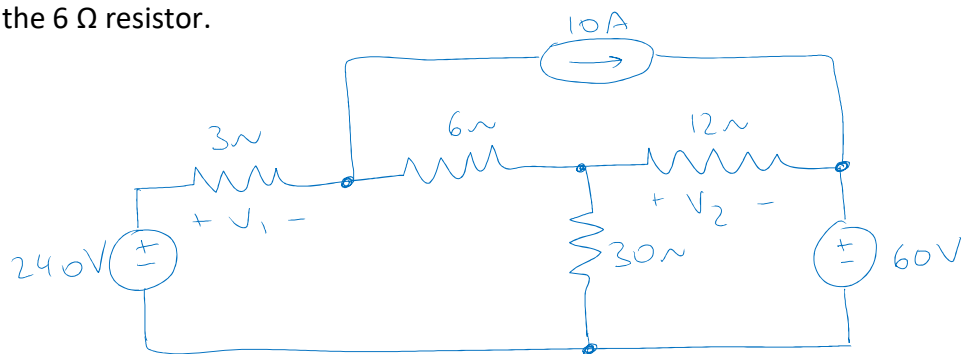For the circuit below: (a) Use nodal analysis to determine v_1 and v_2 . (b) Compute the power absorbed by the $6\ \Omega$ resistor.



Chapter 5, Ex 49: Thevenin equivalent

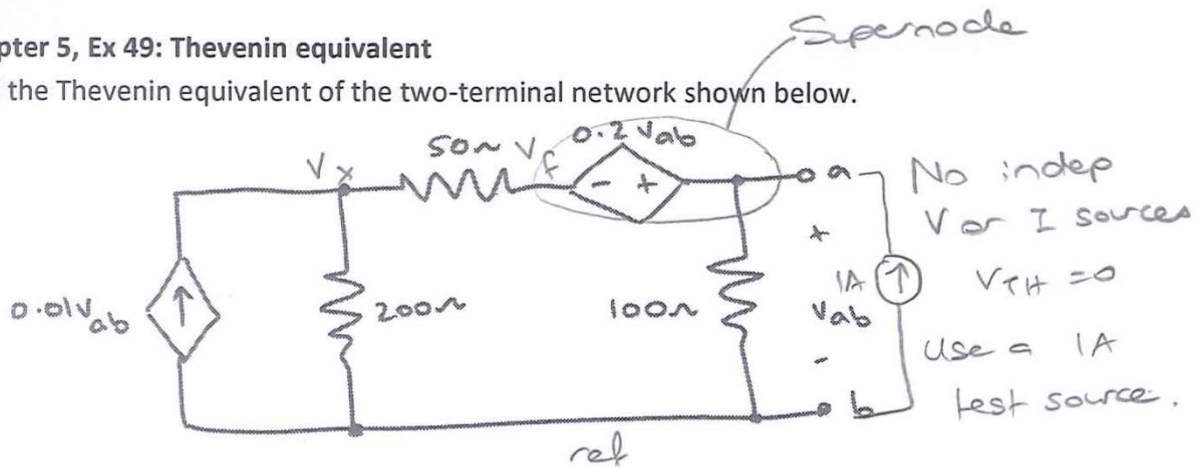Find the Thevenin equivalent of the two-terminal network shown below.



Node x ($\sum I_{out} = 0$)

$$-0.01V_{ab} + \frac{V_x}{200} + \frac{V_x - V_f}{50} = 0$$

Supernode f-a ($\sum I_{out} = 0$)

$$\frac{V_f - V_x}{50} + \frac{V_{ab}}{100} - 1 = 0$$

$$V_{ab} - V_f = 0.2V_{ab}$$

$$V_{ab} = 192.3V$$

$$R_{TH} = \frac{V_{ab}}{1} = 192.3\Omega$$

