


Name:

Student ID:

Pre-tutorial 4 Questions (to be attempted before class on May 3rd, 2019)

Chapter 2, Ex 20: Power absorbed

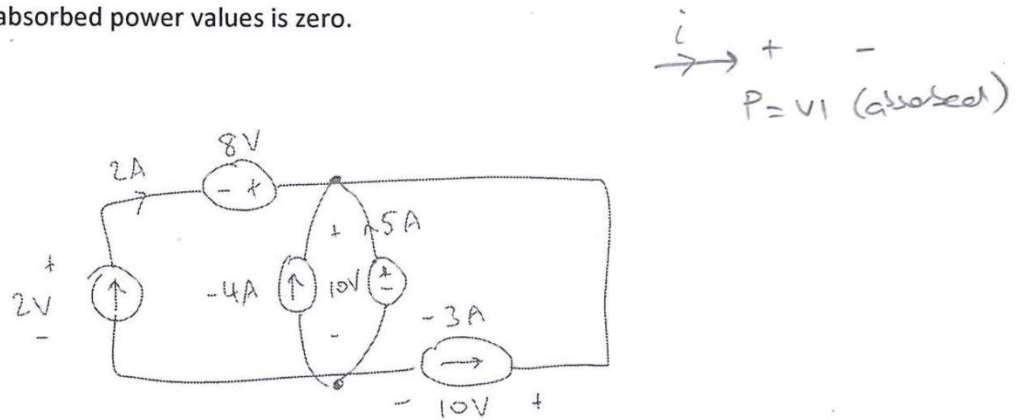Determine which of the five sources are being charged (absorbing positive power), and show that the algebraic sum of the five absorbed power values is zero.



2V source $P = v(-i) = 2 \times (-2) = -4W$ absorbed
or 4W generated.

8V source $P = v(-i) = 8 \times (-2) = -16W$ absorbed
or 16W generated.

-4A source $P = v(-i) = 10 \times (-(-4)) = 40W$ absorbed.

10V source $P = v(-i) = 10 \times (-5) = -50W$ absorbed
or 50W generated

-3A source $P = v(-i) = 10 \times (-(-3)) = 30W$ absorbed.

$$\sum P_{\text{sources}} = 0$$

$$-4 - 16 + 40 - 50 + 30 = 0 \quad \checkmark$$


Conservation of energy.

For power absorbed problems you can also try Ex. 22.

Chapter 7, Ex 11a: Capacitors

The current flowing through a 33 mF capacitor is shown graphically below.

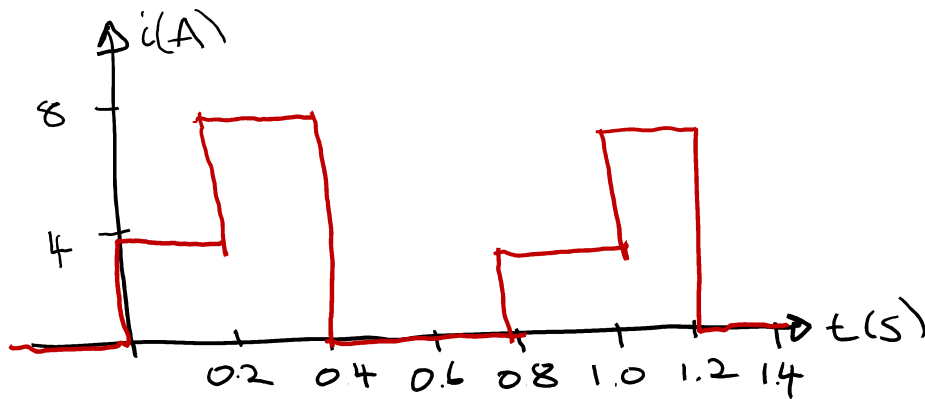- a) Assuming the passive sign convention, sketch the resulting voltage waveform across the device.



Q11a)

$$C = 33 \text{ mF}$$

$$v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

⇒ integral of a horizontal straight line (i.e. a constant) is a constant slope straight line. If find the end-points can just join them.

$$\begin{aligned} \text{@ } t = 0.2: \quad v &= \frac{1}{33 \times 10^{-3}} \int_0^{0.2} 4 dt + 0 \\ &= \frac{4}{33 \times 10^{-3}} [t]_0^{0.2} \\ &= \frac{4 \times 0.2}{33 \times 10^{-3}} \\ &= 24.2 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{@ } t = 0.4: \quad v &= \frac{1}{33 \times 10^{-3}} \int_{0.2}^{0.4} 8 dt + 24.2 \\ &= \frac{8}{33 \times 10^{-3}} [t]_{0.2}^{0.4} + 24.2 \\ &= \frac{8 \times (0.4 - 0.2)}{33 \times 10^{-3}} + 24.2 \\ &= 72.7 \text{ V} \end{aligned}$$

@ $t = 0.8$:
$$v = \frac{1}{33 \times 10^{-3}} \int_{0.4}^{0.8} 0 \, dt + 72.7$$

$$= 72.7 \text{ V}$$

 (or by inspection)

@ $t = 1$:
$$v = \frac{1}{33 \times 10^{-3}} \int_{0.8}^1 4 \, dt + 72.7$$


$$= \frac{4}{33 \times 10^{-3}} [t]_{0.8}^1 + 72.7$$

$$= 97.0 \text{ V}$$

@ $t = 1.2$:
$$v = \frac{1}{33 \times 10^{-3}} \int_1^{1.2} 8 \, dt + 97$$

$$= \frac{8}{33 \times 10^{-3}} [t]_1^{1.2} + 97$$



$$= 145.5 \text{ V}$$

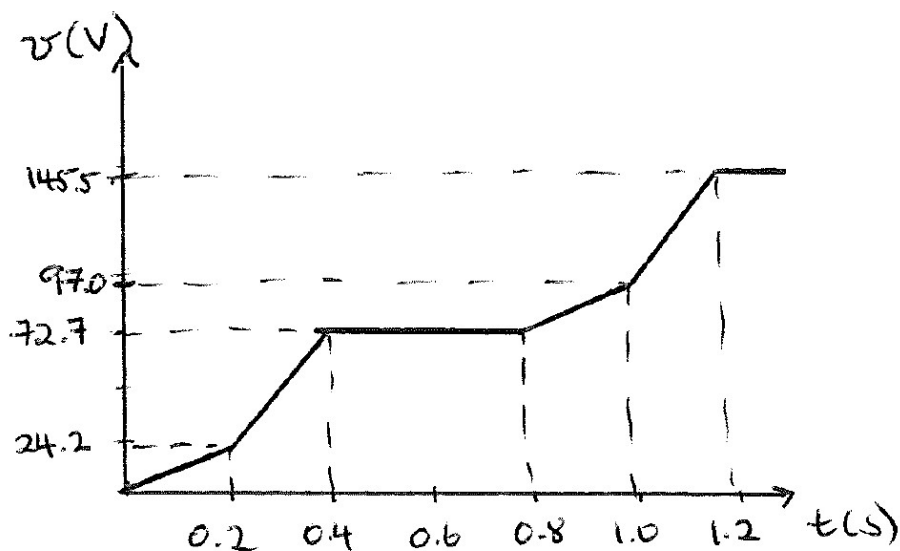

At Tutorial 4 – Marked Question (3rd May 2019)

Chapter 7, Ex 41: Equivalent capacitance/inductance

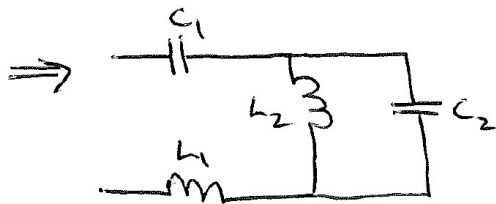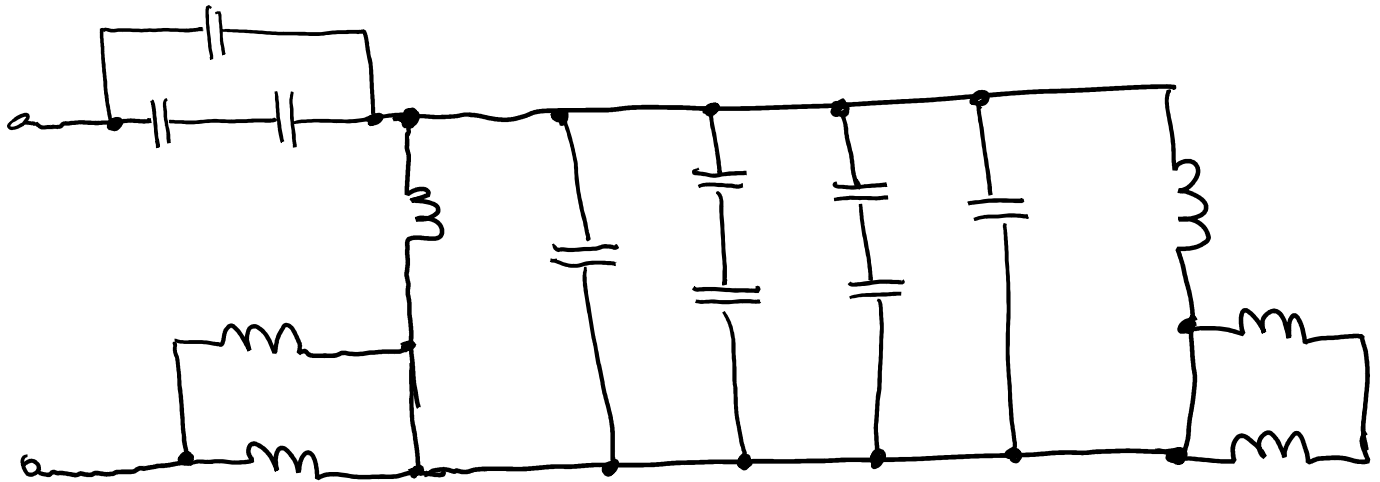Reduce the network below to the smallest possible number of components if each inductor is 1 nH and each capacitor is 1 mF.



$$C_1 = \frac{(1 \times 10^{-3})^2}{1 \times 10^{-3} + 1 \times 10^{-3}} + 1 \times 10^{-3}$$

$$= 1.5 \times 10^{-3} \text{ F}$$


$$C_2 = \left(\frac{(1 \times 10^{-3})^2}{2 \times 10^{-3}} \right) \times 2 + 2 \times 10^{-3}$$

$$= 3 \text{ mF}$$

$$L_2 = 500 \times 10^{-12} \text{ H}$$

$$L_1 = \frac{(1 \times 10^{-9})^2}{1 \times 10^{-9} \times 2}$$


$$= 500 \times 10^{-12} \text{ H}$$

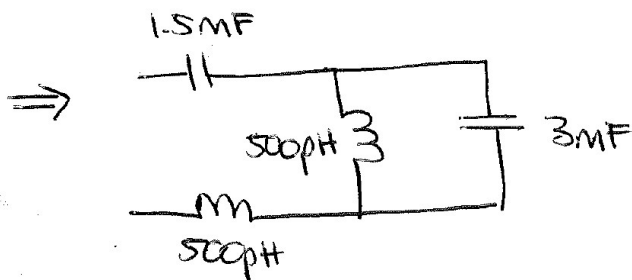


At Tutorial 4 – Unmarked Questions (3rd May 2019)

Ch 5 ex 61: Maximum power transfer

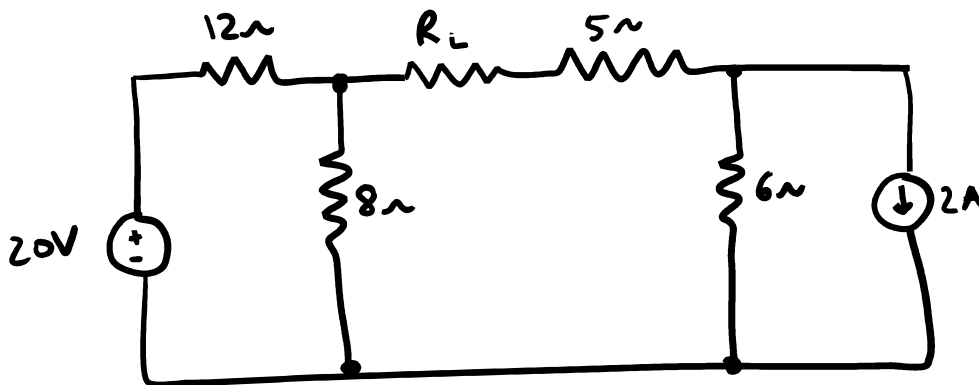Given you can select any value of R_L , what is the maximum power that could be delivered to R_L ?




1) Find Thévenin equivalent resistance:

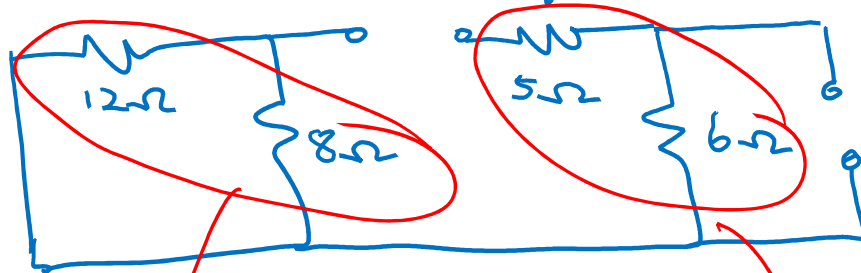


parallel

series
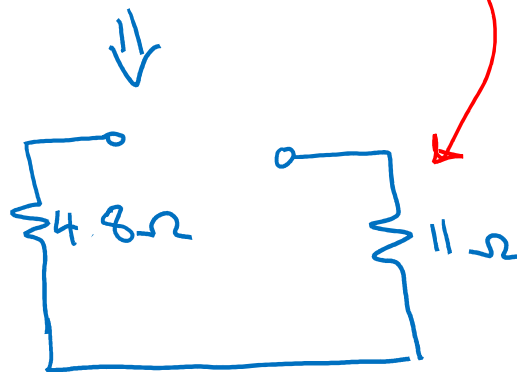
$$12 \parallel 8 = \frac{12 \times 8}{12 + 8} = 4.8 \Omega$$





$$R_{Th} = 11 + 4.8 = 15.8 \Omega$$

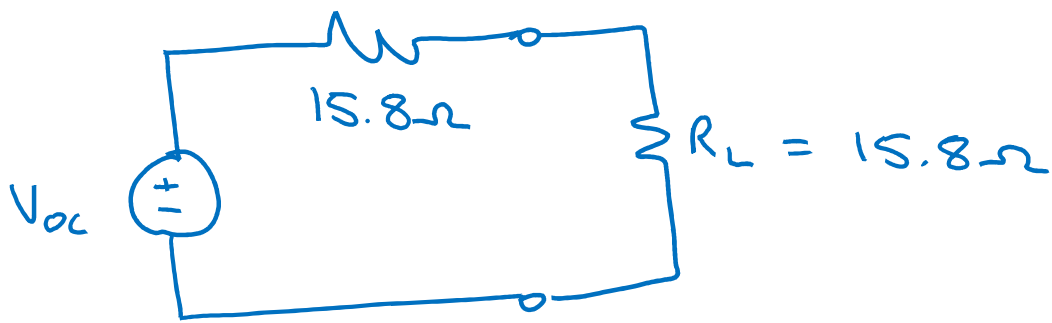



For Max pwr transfer, $R_L = R_{TH}$

2) Find V_{oc} using superposition:

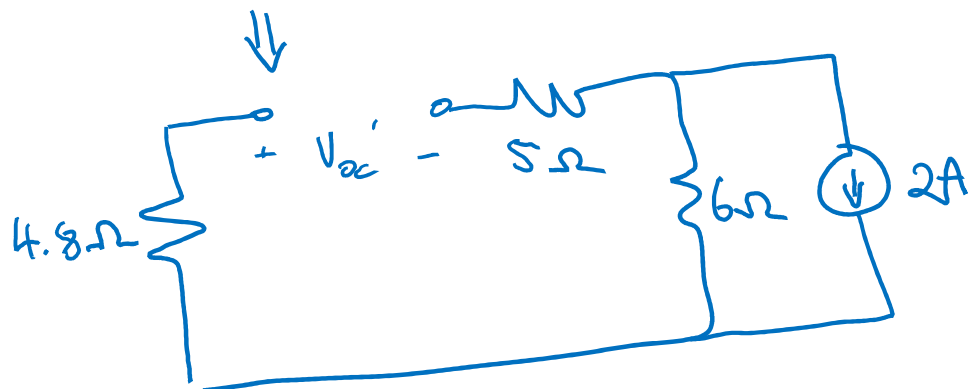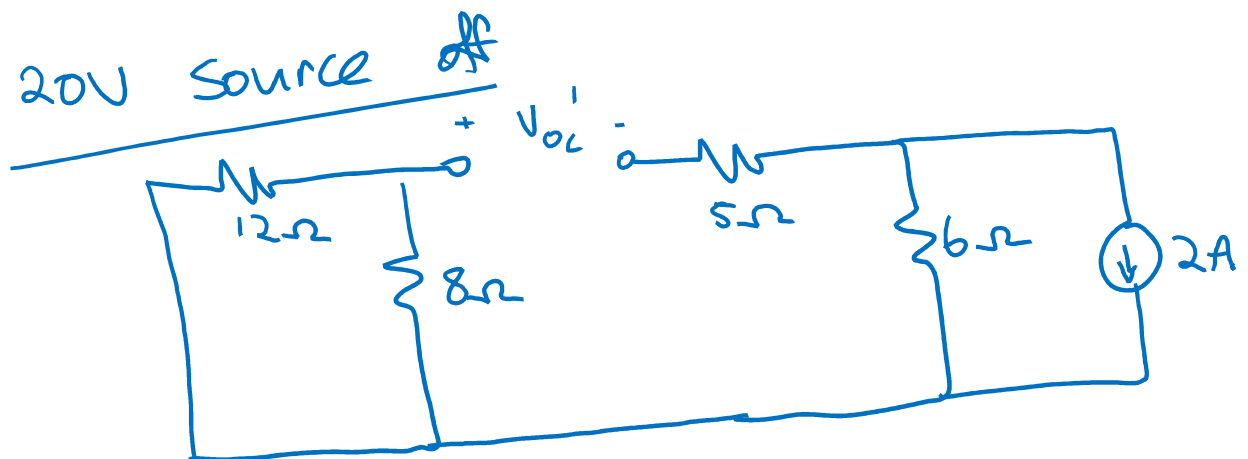


All current goes through 6Ω resistor,
 $\therefore V_{oc}' = 6 \times 2 = 12V$

2A source

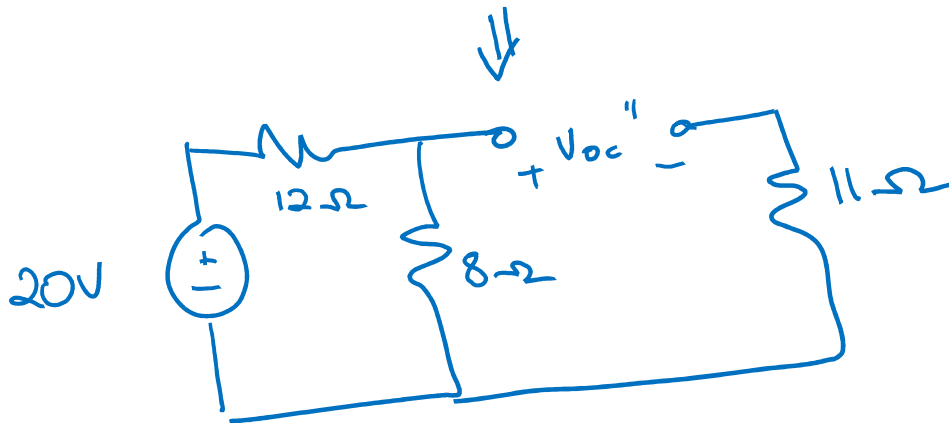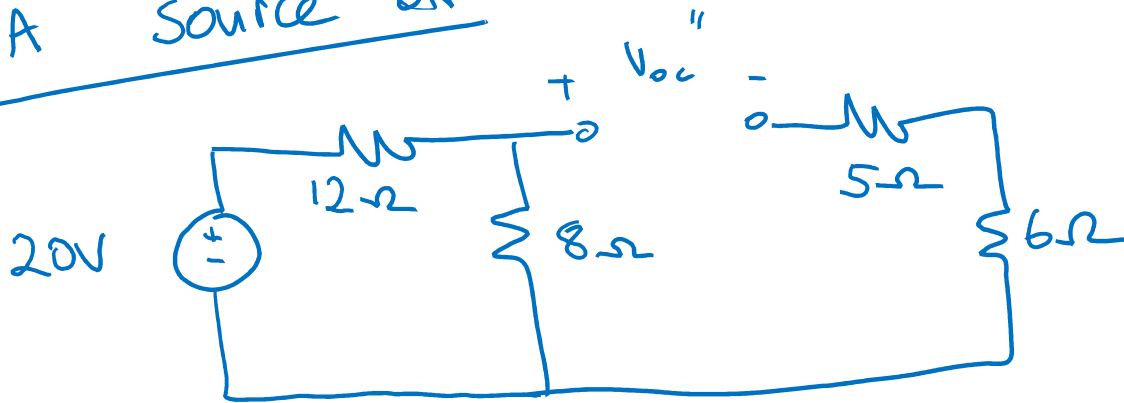

$$V_{8\Omega} = V_{oc}'' = \frac{20 \times 8}{12 + 8} = 8V$$
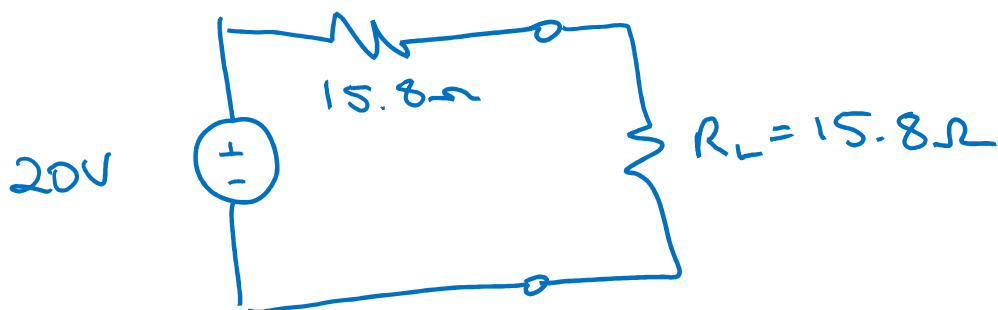
$$\therefore V_{oc} = V_{oc}' + V_{oc}'' = 12 + 8 = 20V$$




$$P = \frac{V^2}{R} = \frac{(20/2)^2}{15.8} = 6.33W$$


Chapter 7, Ex 14: Power

Assume the circuits below have been connected for a long time. Calculate the power dissipated in the $40\ \Omega$ resistor and the voltage labeled v_c in the circuits below:

a)

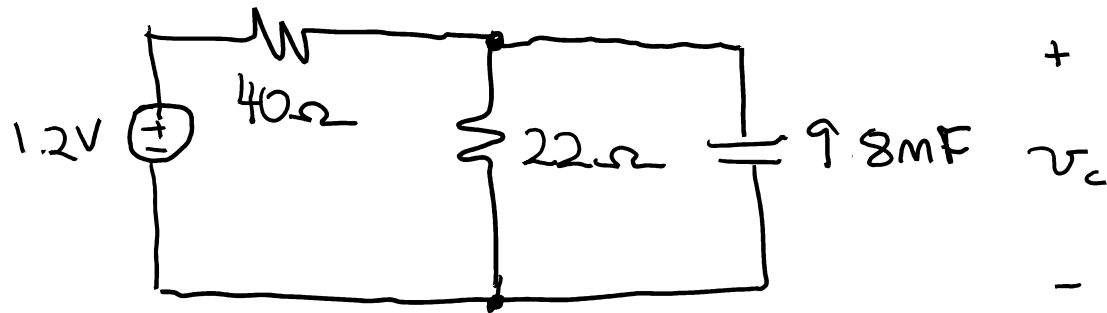

capacitor acts as an open circuit to DC

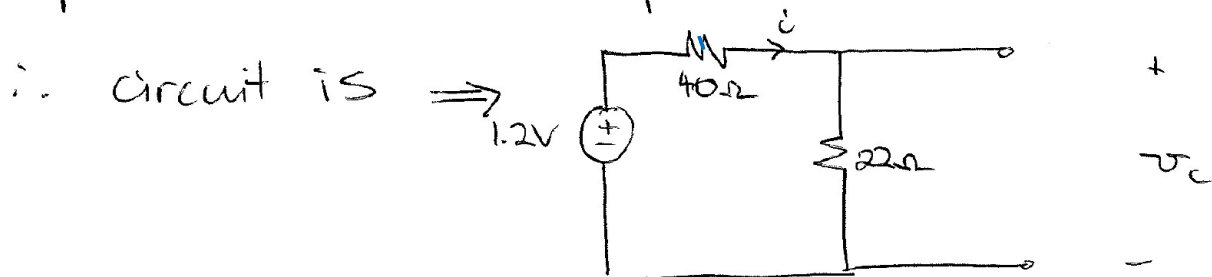


$$i = \frac{1.2}{(40+22)}$$
$$= 19\text{mA}$$


$$P_{40\ \Omega} = i^2 R$$
$$= (19 \times 10^{-3})^2 \times 40$$
$$= 14.98\text{mW}$$

$$v_c = iR$$
$$= 19 \times 10^{-3} \times 22$$
$$= 0.43\text{V}$$

b)

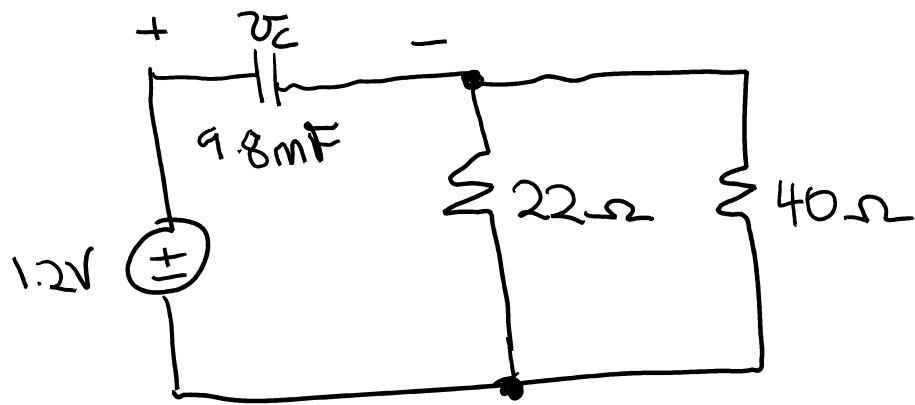

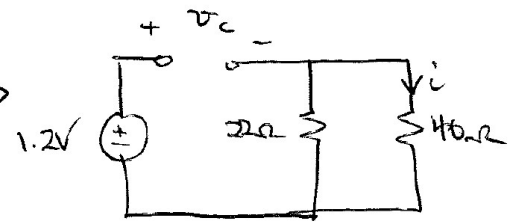as above, \therefore circuit becomes \Rightarrow



$$P_{40\Omega} = 0W \quad (i = 0A)$$

$$v_C = 1.2V$$

Chapter 7, Ex 27: Inductors

Determine the amount of energy stored in a 33 mH inductor at $t = 1$ ms as a result of a current i_L given by:

a) 7 A

$$i = 7A$$

$$W_L = \frac{1}{2} L i^2$$

$$= \frac{1}{2} \times 33 \times 10^{-3} \times 7^2$$

$$= 808.5 \text{ mJ}$$

b) $3 - 9e^{-10^3 t}$ mA

$$i = 3 - 9e^{-10^3 t} \text{ mA}$$

$$W_L = \frac{1}{2} L i^2$$

$$= \frac{1}{2} \times 33 \times 10^{-3} \times (3 \times 10^{-3} - 9e^{-10^3 t} \times 10^{-3})^2$$

$$= 16.5 \times 10^{-3} (3 \times 10^{-3} - 3.3 \times 10^{-3})^2$$

$$= 16.5 \times 10^{-3} \times 96.67 \times 10^{-9}$$

$$= 1.595 \text{ nJ}$$

Chapter 7, Ex 25: Inductors

The voltage across a 2 H inductor is given by $v_L = 4.3t$, $-0.1 \text{ s} \leq t \leq 50 \text{ ms}$. Knowing that $i_L(-0.1) = 100 \mu\text{A}$, calculate the current (assuming it is defined consistent with the passive sign convention) as t equal to:

a) 0

b) 1.5 ms

c) 45ms

$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

$$= \frac{1}{2} \left[\int_{-0.1}^t 4.3\tau d\tau \right] + 100 \times 10^{-6}$$

$$= \frac{1}{2} \times 4.3 \int_{-0.1}^t \tau d\tau + 100 \times 10^{-6}$$

$$= 2.15 \left[\frac{1}{2} \tau^2 \right]_{-0.1}^t + 100 \times 10^{-6}$$

$$= 2.15 \left(\frac{1}{2} t^2 - 5 \times 10^{-3} \right) + 100 \times 10^{-6}$$

$$a) i(0) = -2.15 \times 5 \times 10^{-3} + 100 \times 10^{-6} = -10.65 \text{ mA}$$

$$b) i(1.5 \text{ ms}) = 2.15 \left(\frac{1}{2} \times (1.5 \times 10^{-3})^2 - 5 \times 10^{-3} \right) + 100 \times 10^{-6} \\ = -10.65 \text{ mA}$$

$$c) i(45 \text{ ms}) = 2.15 \left(\frac{1}{2} (45 \times 10^{-3})^2 - 5 \times 10^{-3} \right) + 100 \times 10^{-6} \\ = -8.47 \text{ mA}$$