


Name:

Student ID:

Pre-tutorial 5 Questions (to be attempted before class on May 17th, 2019)

Chapter 8, Ex 20: Source-free RC circuit

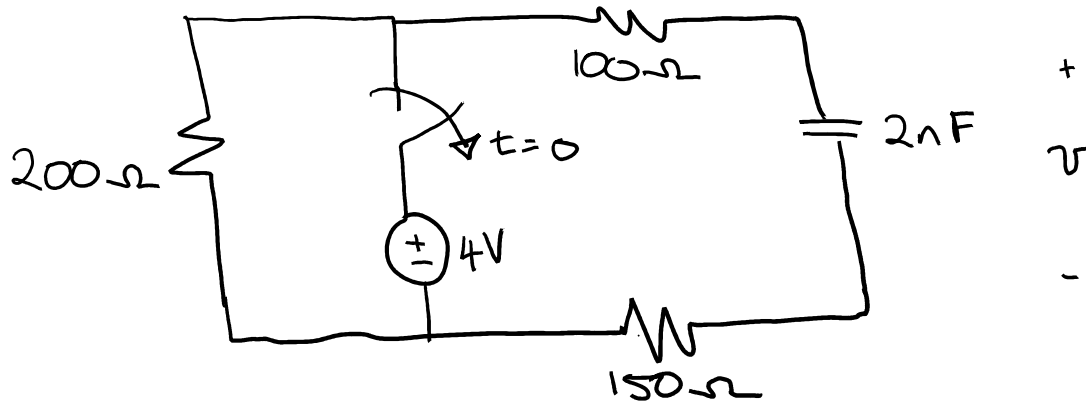
The switch drawn in the circuit below has been closed for such a long time that any transients which might have arisen from first connecting the voltage source have disappeared.



a) Determine the circuit time constant

$$\tau = RC$$


For $t > 0$ circuit is:

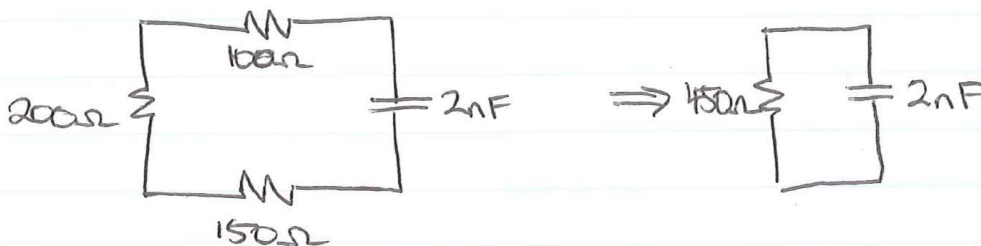

$$\begin{aligned} RC &= 150 \times 2 \times 10^{-9} \\ &= 900 \text{ ns} \end{aligned}$$

b) Calculate the voltage $v(t)$ at $t = \tau, 2\tau$, and 5τ

$t < 0$:

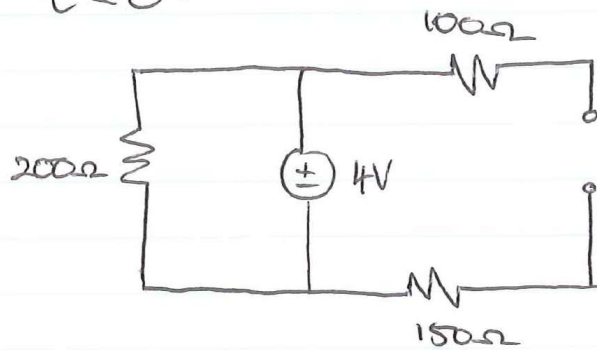

$$v_c(0^-) = 4V$$

$$v_c(0^-) = v_c(0^+) = 4V$$

$$\begin{aligned} \text{For } t > 0: \quad v(t) &= Ae^{-t/\tau} \\ &= Ae^{-t/900 \times 10^9} \\ &= Ae^{-1.11 \times 10^6 t} \end{aligned}$$

$$\begin{aligned} v(0) &= Ae^{-1.11 \times 10^6 \times 0} = 4 \\ A &= 4 \end{aligned}$$

$$\therefore v(t) = 4e^{-1.11 \times 10^6 t} \text{ V} \quad t > 0$$


$$\begin{aligned} v(\tau) &= 4e^{-1} \\ &= 1.47 \text{ V} \end{aligned}$$

$$\begin{aligned} v(2\tau) &= 4e^{-2} \\ &= 0.54 \text{ V} \end{aligned}$$


$$\begin{aligned} v(5\tau) &= 4e^{-5} \\ &= 0.027 \text{ V} \end{aligned}$$

Chapter 8, Ex 49: Driven RL circuit

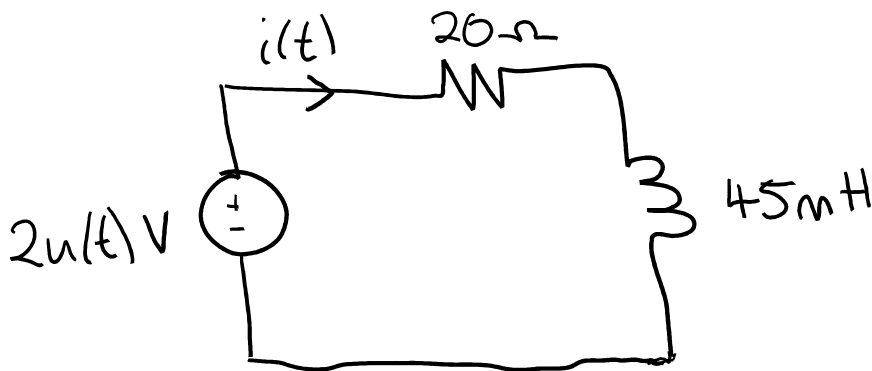The circuit shown below is powered by a source which is inactive for $t < 0$. Obtain an expression for $i(t)$ valid for all t .




For $t < 0$:

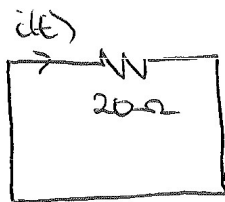


$$i(t) = 0 \text{ A}$$

For $t > 0$, forcing function circuit:

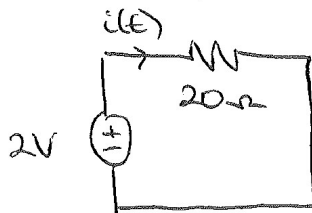

$$i_F(t) = \frac{2}{20} = 0.1 \text{ A}$$

For $t > 0$, natural function circuit:

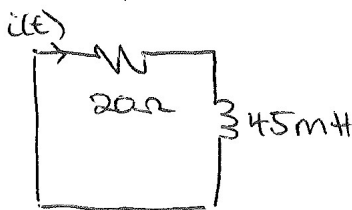

$$i_n(t) = I_0 e^{-t/\tau}$$

$$i_n(t) = I_0 e^{-444.4t}$$

$$\begin{aligned} \tau &= \frac{L}{R} \\ &= \frac{45 \times 10^{-3}}{20} \\ &= 2.25 \times 10^{-3} \text{ s} \\ \frac{1}{\tau} &= 444.4 \text{ s}^{-1} \end{aligned}$$


$$\begin{aligned} i(t) &= i_F(t) + i_n(t) \quad t > 0 \\ &= 0.1 + I_0 e^{-444.4t} \end{aligned}$$

$$\begin{aligned} i(0^-) = i(0^+) &= 0 & i(0) &= 0.1 + I_0 = 0 \\ & & I_0 &= -0.1 \end{aligned}$$

$$\begin{aligned} i(t) &= 0.1 - 0.1 e^{-444.4t} \text{ A} \quad t > 0 \\ &= 0.1 (1 - e^{-444.4t}) u(t) \text{ A} \end{aligned}$$


At Tutorial 5 – Marked Question (17th May 2019)

Chapter 8, Ex 8: Source-free RL circuit

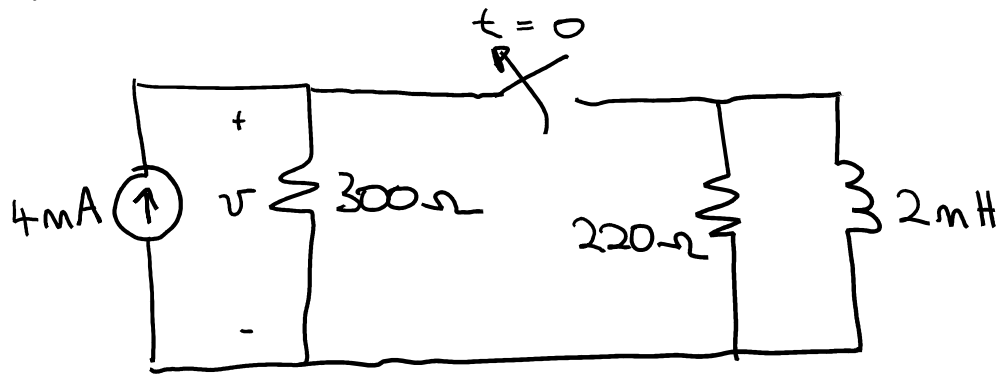

The switch in the circuit above has been closed a very long time. Calculate the voltage v as well as the energy stored in the inductor at:

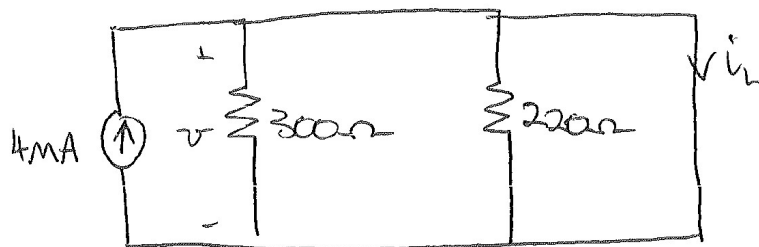- a) The instant just prior to the switch being thrown open




$$i_L(0^-) = 4\text{mA}$$

$$v(0^-) = 0\text{V}$$

$$\begin{aligned} \omega(0^-) &= \frac{1}{2} L i^2 \\ &= \frac{1}{2} \times 2 \times 10^{-3} \times (4 \times 10^{-3})^2 \\ &= 16 \times 10^{-9} \text{ J} \end{aligned}$$

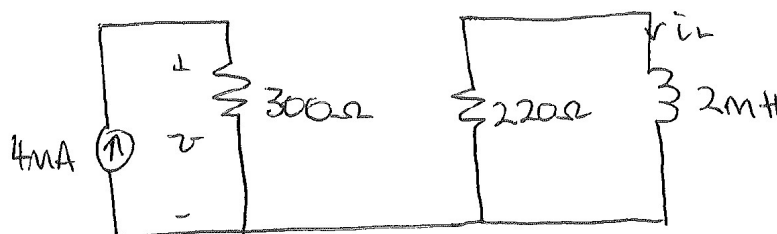- b) The instant just after the switch is opened



$$\begin{aligned} v(0^+) &= 4 \times 10^{-3} \times 300 \\ &= 1.2\text{V} \end{aligned}$$

$$i_L(0^+) = i_L(0^-) = 4\text{mA}$$

$$\begin{aligned} \omega_L(0^+) &= \frac{1}{2} \times 2 \times 10^{-3} \times (4 \times 10^{-3})^2 \\ &= 16 \times 10^{-9} \text{ J} \end{aligned}$$

c) $t = 8 \mu s$

$$v(8 \mu s) = v(0^+) = 1.2V$$

$$i = I_0 e^{-t/\tau}$$

$$= 4 \times 10^{-3} e^{-110 \times 10^3 t}$$

$$\frac{1}{\tau} = \frac{R}{L}$$

$$= \frac{220}{2 \times 10^{-3}}$$

$$= 110 \times 10^3$$

$$i(8 \mu s) = 4 \times 10^{-3} e^{-110 \times 10^3 \times 8 \times 10^{-6}}$$

$$= 1.66 \text{ mA}$$


$$w(8 \mu s) = \frac{1}{2} \times 2 \times 10^{-3} \times (1.66 \times 10^{-3})^2$$

$$= 2.7 \times 10^{-9} \text{ J}$$


At Tutorial 5 – Unmarked Question (17th May 2019)

Chapter 8, Ex 60: Driven RC circuit

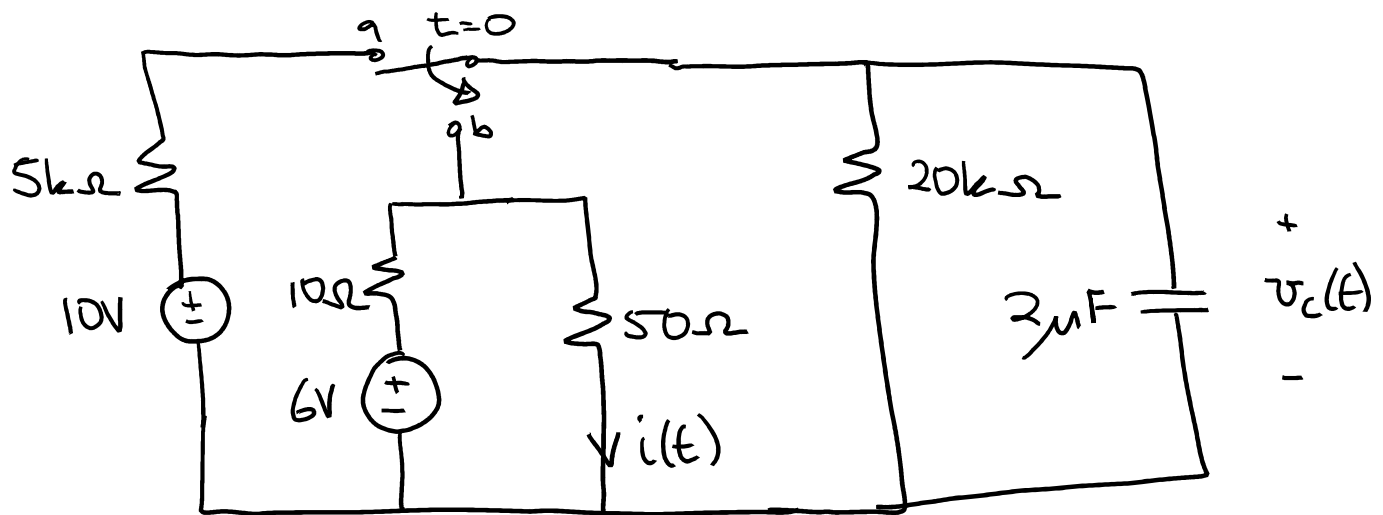The switch shown in the circuit below has been in position *a* since the original Battlestar Galactica aired on TV. It is moved to position *b* at time $t = 0$. Obtain expressions for $i(t)$ and $v_c(t)$ valid for all values of t .




$t < 0$:

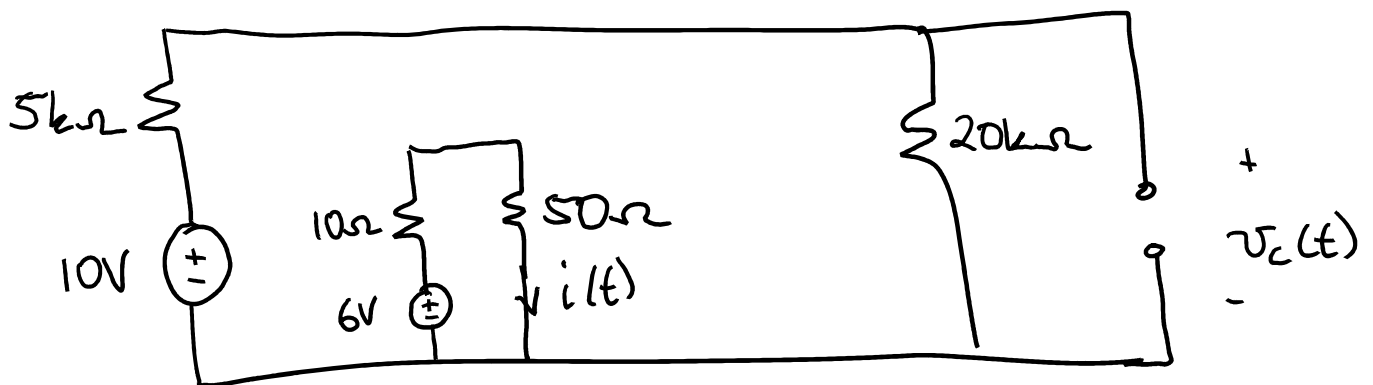


$$i(0^-) = \frac{6}{60} = 0.1 \text{ A}$$

$$v_c(0^-) = 10 \times \frac{20}{25} \text{ (voltage divider)} = 8 \text{ V}$$

$t > 0$ (forced):

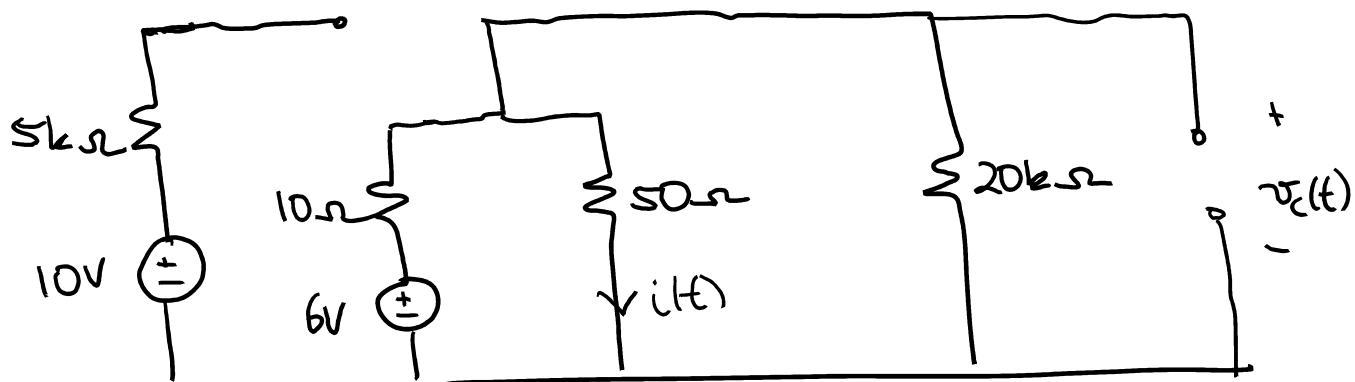

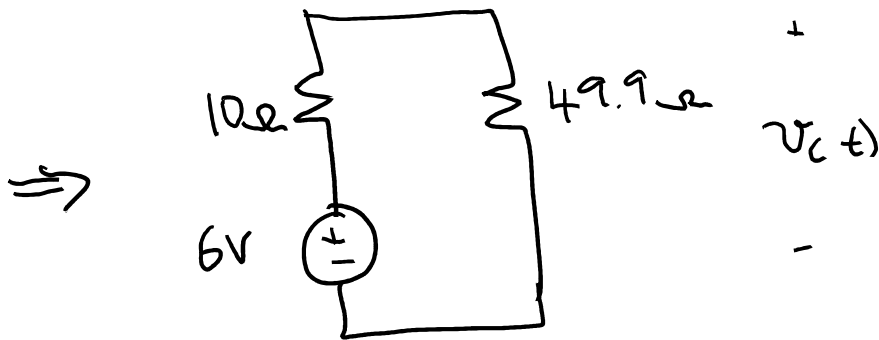

$$R_{eq} = \frac{50 \times 20k}{50 + 20k}$$


$$= 49.9\Omega$$

$$v_{c,F} = 6 \times \frac{49.9}{59.9} \text{ (voltage divider)}$$

$$= 5V$$

$$i_F = 5/50 = 0.1A$$

$t > 0$, natural:

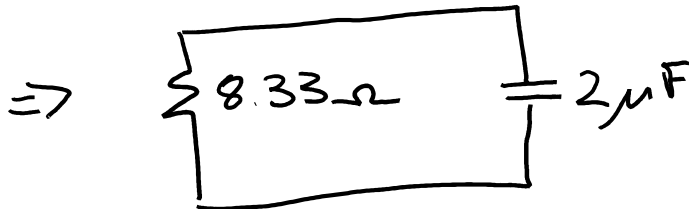

$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{50} + \frac{1}{20k}$$

$$R_{eq} = 8.33\Omega$$

$$v_{c,n} = V_0 e^{-t/\tau}$$

$$\tau = RC$$

$$\frac{1}{\tau} = \frac{1}{8.33 \times 2\mu}$$

$$= 60 \times 10^3 \text{ s}^{-1}$$

$$v_{c,n} = V_0 e^{-60 \times 10^3 t}$$

$$v_c = v_{c,F} + v_{c,n} \quad t > 0$$

$$= 5 + V_0 e^{-60 \times 10^3 t}$$

$$v_c(0^-) = v_c(0^+) = 8$$

$$v_c(0) = 5 + V_0 = 8$$

$$V_0 = 3$$

$$v_c = \begin{cases} 8 \text{ V} & t \leq 0 \\ 5 + 3e^{-60 \times 10^3 t} & t > 0 \end{cases}$$

$$= 8 - 3(1 - e^{-60 \times 10^3 t}) u(t) \text{ V}$$

$$i(t) = v/r$$

$$= \frac{5 + 3e^{-60 \times 10^3 t}}{50} \quad t > 0$$

$$= 0.1 + 0.06e^{-60 \times 10^3 t} \text{ A} \quad t > 0$$

$$= \begin{cases} 0.1 \text{ A} & t \leq 0 \\ 0.1 + 0.06e^{-60 \times 10^3 t} \text{ A} & t > 0 \end{cases}$$