

## Term 3 Additional Tutorial Questions


These are tutorial questions that I wrote when I first lectured Term 3. I have since converted to questions from the textbook to be consistent with the other terms. However, the below could be useful for your exam study ☺

### 1. Complex Numbers

Let  $z_1 = 10 + j15$  and  $z_2 = -4 + j3$


- Convert  $z_1$  and  $z_2$  to polar notation  $z = re^{j\theta}$  using Pythagoras and trigonometry (i.e. not just the calculator function to convert between forms).  $\theta$  is to be in radians, not degrees.
- Work out  $z_1/z_2$  and  $z_1 - z_2$
- Let  $z_3 = r_3 e^{j\theta_3}$  and  $z_4 = r_4 e^{j\theta_4}$ . Show that  $z_3 z_4 = r_3 r_4 e^{j(\theta_3 + \theta_4)}$

### 2. Phasors

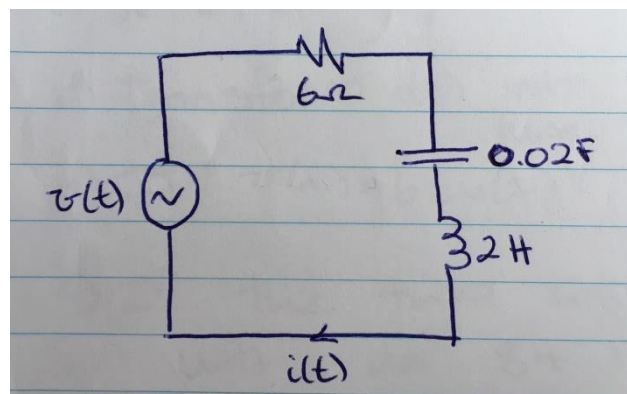

For the circuit above, if  $v(t) = 10 \cos(7t + 30^\circ) V$ , what is  $i(t)$ ? Use phasors to calculate the answer. Ignore initial conditions.

### 3. Phasors

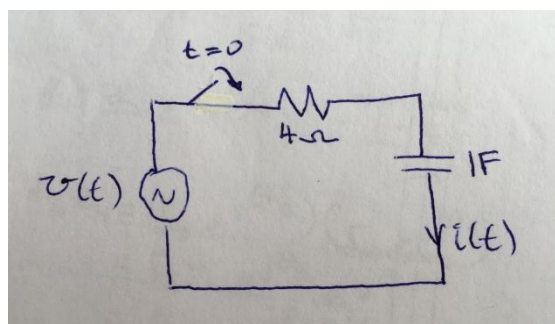

For the circuit to the left,  $v(0^-) = 0V$  and  $v(t) = 20 \cos(2t + \pi) V$ . What is  $i(t)$ ?

(See hints on the following page.)

Hints:

- Write an equation for  $v(t)$  using KVL, and write equations for  $\mathbf{V}$  and  $\mathbf{I}$
- Replace the time-domain functions in the first equation with phasors
- Rearrange so have  $\mathbf{I} =$
- Simplify
- Convert phasors back into time-domain variables


4. Laplace Transform

- Using the one-sided LT formula, find the LT of  $f(t) = 2u(t - 6) + e^{-4t}$
- Using the tables, find the LT of  $f(t) = 7\delta(t) + 9tu(t)$
- For the circuit in Q2, write an equation for  $I(s)$  if  $v(t) = tu(t)$  and  $i(0) = 0A$ . Write it in the form  $I(s) = \frac{x+ys+zs^2}{a+bs+cs^2}$ . Note some of the coefficients could equal zero.

5. Laplace Transform

Show that  $\mathcal{L}[\sin(\omega t) u(t)] = \frac{\omega}{s^2 + \omega^2}$  by using  $\sin(\omega t) = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$ . Do not use the tables.

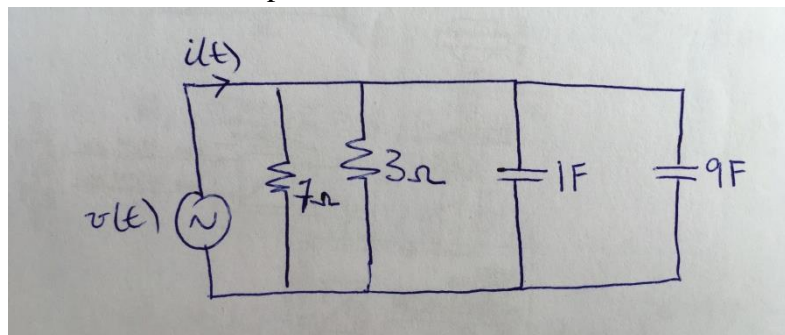6. Laplace Transform and Inverse Laplace Transform



For the circuit above, all initial conditions = 0.

- Simplify the circuit so there is only one capacitor and one resistor.
- Write an equation for  $i(t)$  using KCL.
- Transform  $i(t)$  into the s-domain (i.e. find  $I(s)$ ). Use the tables for this.
- If  $v(t) = 6tu(t)V$  find  $i(t)$  from  $I(s)$  for  $t > 0$ .
- If the two capacitors were replaced with an  $8H$  inductor, what would  $i(t)$  be? You will need to repeat the above process. Remember for an inductor  $i(t) = \frac{1}{L} \int_{t_0}^t v(t') dt' + i(t_0)$


7. Inverse Laplace Transform

- a) Using partial fractions, find the inverse LT of  $I(s) = \frac{7}{s^2 + s - 12}$
- b) Find the simplified equation for  $V(s) = \frac{s+2}{(s^2+4)(s+1)}$  using partial fractions

8. Laplace Transform and Inverse Laplace Transform


- a) If  $v(t) = \delta(t-3)u(t-3) + 8e^{-(t-4)}u(t-4)$  V, find  $V(s)$ . Hint: Use the tables and time delay
- b) Using the IVT, find  $v(0^+)$  of  $v(t) = (e^{-3t} + t)u(t)$  V

9. s-domain Analysis

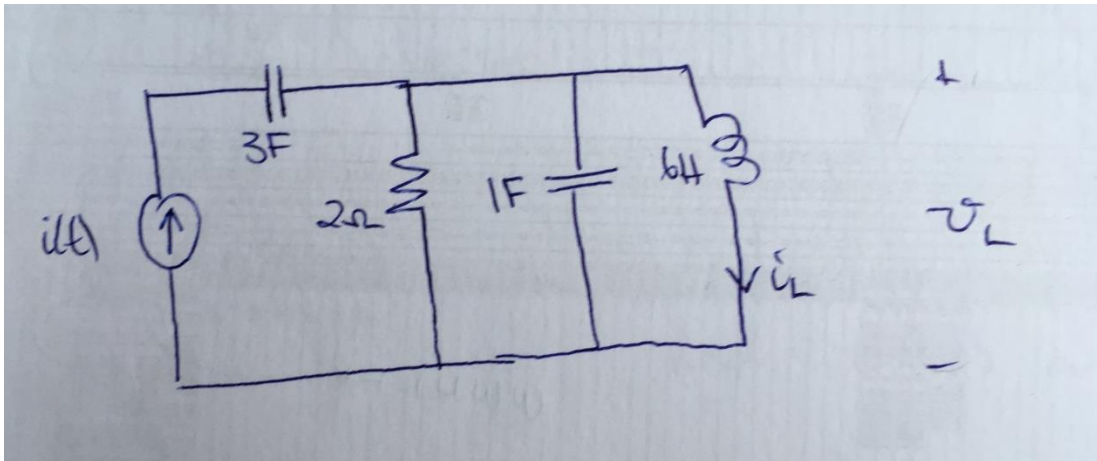

- a) Redraw the circuit above in the s-domain if  $i(t) = \sin(2t)u(t)$  A, and the initial conditions are all 0.
- b) Redraw the circuit above in the s-domain if  $i_L(0^-) = 2$  A and  $v_L(0^-) = 6$  V. Use a voltage source model where required, not a current source model.

10. s-Domain Analysis

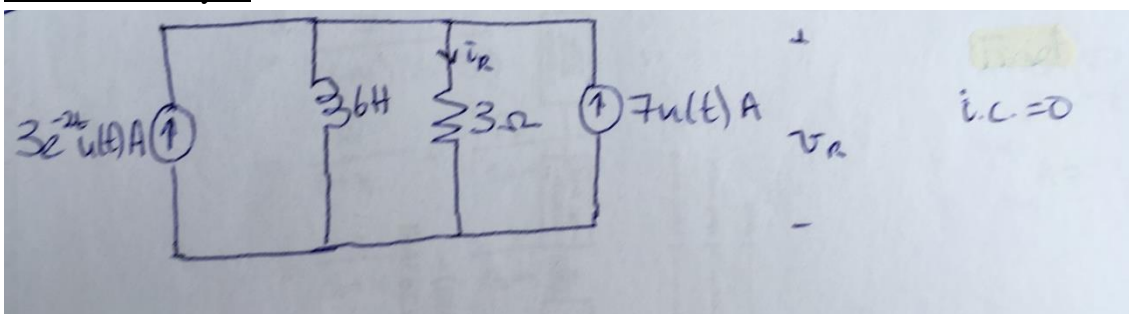

- a) For the circuit above, write an equation for the currents in the circuit using KCL.

Carry out a LT on this equation. Rearrange to the form  $I_R(s) = \frac{N(s)}{D(s)}$ .


$$\text{Hint: } i_L = \frac{1}{L} \int_0^t v_L dT + i_L(0^-).$$

- b) Using partial fractions and the LT tables, find the inverse LT of  $I_R(s)$ , thus finding  $i_R(t)$ .

11. Initial value Theorem and Final Value Theorem


$V(s) = \frac{s(s+3)}{s^2+4s+4}$ . Use the IVT and the FVT to find  $v(0^+)$  and  $v(\infty)$ .

12. s-Domain Circuits

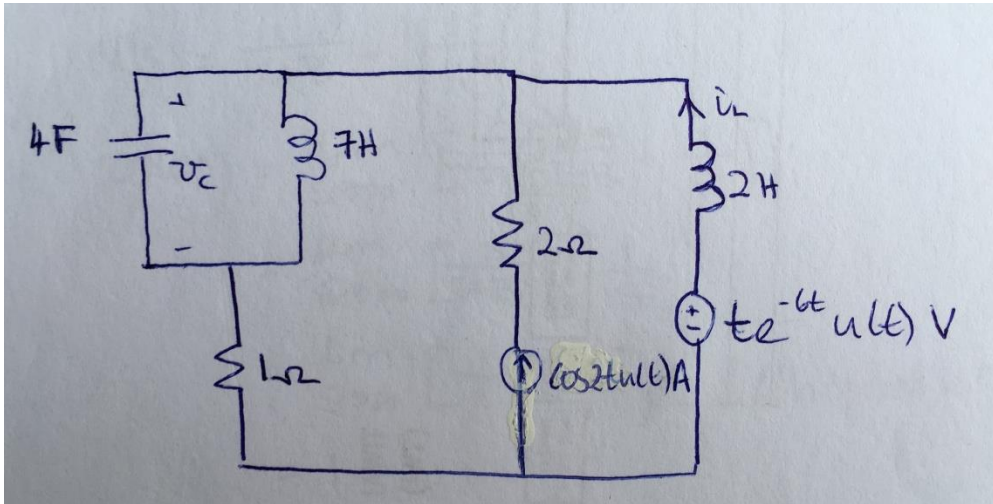

Redraw the circuit above in the s-domain, using a current source for the capacitor and a voltage source for the inductor.  $v_c(0^-) = 2V$ ,  $i_L(0^-) = 1A$ , no i.c. across 7H inductor.

13. s-Domain Circuit Analysis

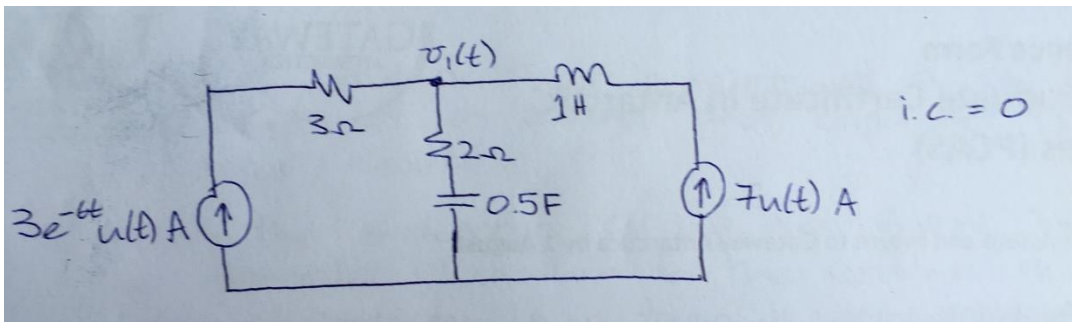

- Draw the above circuit in the s-domain.
- Write an equation for the node  $V_1(s)$  and simplify it.
- Use partial fractions to prepare for the inverse LT.
- Take the inverse LT to get  $v_1(t)$ .

14. Impulse Response, Transfer Function, and Convolution

- If the input to a system is  $x(t) = 6tu(t) - 2u(t - 4)$ , and the impulse response  $h(t) = 7u(t)$ , what is the output  $y(t)$ ? Hint: Work in the s-domain, and find the convolution of  $x(t)$  and  $h(t)$
- What if  $h(t) = 9u(t - 2)$ ?

15. Poles, Zeros, and Transfer Functions

- a) If  $H(s) = \frac{2s^2+12s}{s^2-3s-28}$  what are its poles and zeroes? Sketch the pole-zero diagram.
- b) Do the same for  $H(s) = \frac{1}{10s^2+6s+1}$ . What is the shape of the system response in this case? (e.g. sinusoid, exponentially decreasing sinusoid, exponentially increasing sinusoid, DC exponential)

16. Transfer Functions


Consider a network that consists of a series combination of a resistor, a capacitor, and a voltage source.

- a) Draw the s-domain circuit, and show that if a voltage is applied at the voltage source, then the transfer function for the voltage across the capacitor is  $H(s) = \frac{1}{RC} \frac{1}{s + (1/RC)}$ .
- b) Find the pole(s) of  $H(s)$ .
- c) Calculate the output response,  $v_{out}(t)$ , if  $v_{in}(t) = 2u(t)$  V.

17. Poles, Zeros, Impulse Response

If  $H(s) = \frac{s^2+4s-6}{s^3+2s^2-15s}$  what are the poles and zeroes of  $H(s)$ , and what is the impulse response  $h(t)$ ?

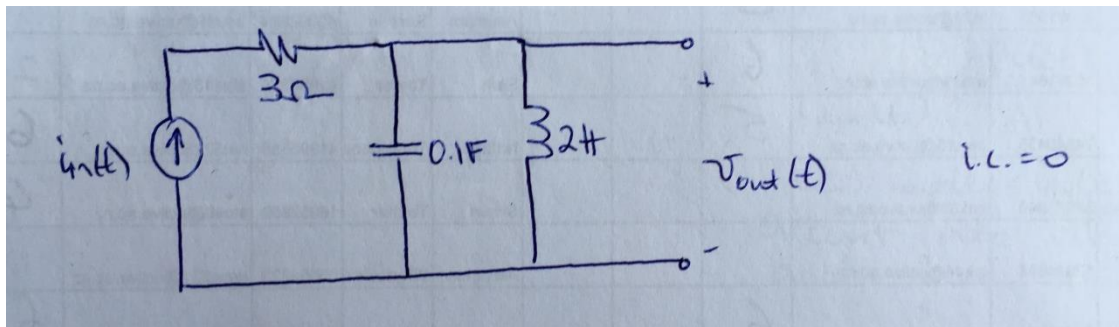18. Transfer Function, Poles, Zeros, Convolution



- a) Find the transfer function  $H(s)$  of the circuit above, the poles and zeroes of  $H(s)$ , and sketch the pole-zero plot.
- b) If  $i_{in}(t) = 6\delta(t)$  A, what is  $v_{out}(t)$ ?