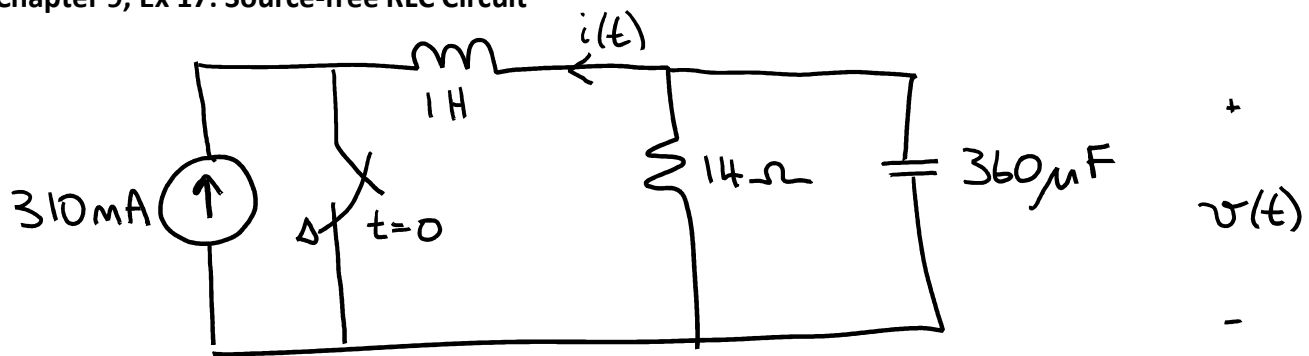


Name:

Student ID:


Pre-tutorial 6 Questions (to be attempted before class on May 31st, 2019)

Chapter 9, Ex 17: Source-free RLC Circuit




Obtain expressions for the current $i(t)$ and voltage $v(t)$ as labelled in the circuit above, which are valid for all $t > 0$.

$t < 0$:

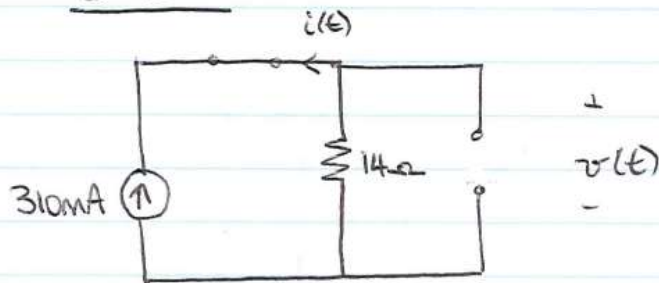

$$\begin{aligned} i(0^-) &= -310 \text{ mA} \\ v(0^-) &= 310 \times 10^{-3} \times 14 \\ &= 4.34 \text{ V} \end{aligned}$$

$t > 0$:

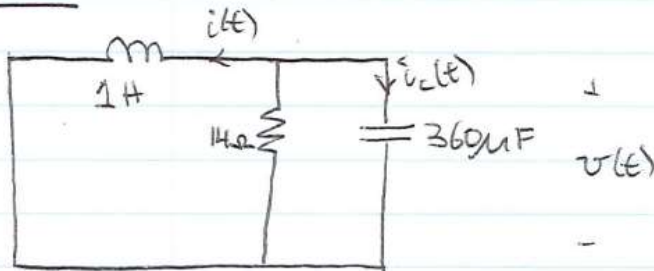

$$\begin{aligned} \alpha &= \frac{1}{2RC} \\ &= \frac{1}{2 \times 14 \times 360 \times 10^{-6}} \\ &= 99.2 \text{ s}^{-1} \end{aligned}$$

$$\begin{aligned} \omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{1 \times 360 \times 10^{-6}}} \\ &= 52.7 \text{ rad/s} \end{aligned}$$

$\alpha > \omega_0$ \therefore overdamped

$$\Rightarrow v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\begin{aligned}
 s_1, s_2 &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \\
 &= -99.2 \pm \sqrt{99.2^2 - 52.7^2} \\
 &= -15.16, -183.24
 \end{aligned}$$

$$v(t) = A_1 e^{-15.16t} + A_2 e^{-183.24t}$$

$$v(0^+) = v(0^-) = 4.34 = A_1 + A_2$$

$$i(0^-) = i(0^+) = -310 \times 10^{-3}$$

$$i_c = C \frac{dv}{dt}$$

$$= 360 \times 10^{-6} (-15.16 A_1 e^{-15.16t} - 183.24 A_2 e^{-183.24t})$$

$$i_c(0^+) = 360 \times 10^{-6} (-15.16 A_1 - 183.24 A_2) = -5.46 \times 10^{-3} A_1 - 0.066 A_2$$

$$i(t) + \frac{v(t)}{14} + i_c(t) = 0$$

$$@ t=0: -310 \times 10^{-3} + \frac{4.34}{14} - 5.46 \times 10^{-3} A_1 - 0.066 A_2 = 0$$

$$-5.46 \times 10^{-3} A_1 - 0.066 A_2 = 0$$

$$A_1 + A_2 = 4.34 \text{ (from previous page)}$$

$$-5.46 \times 10^{-3} (4.34 - A_2) - 0.066 A_2 = 0$$

$$-0.06 A_2 = 0.0237$$

$$A_2 = -0.391$$

$$\begin{aligned}
 A_1 &= 4.34 - (-0.391) \\
 &= 4.73
 \end{aligned}$$

$$v(t) = 4.73 e^{-15.16t} - 0.391 e^{-183.24t} \quad \forall \quad t > 0$$

$$i(t) = -\frac{v(t)}{14} - i_c(t)$$

$$= -0.34 e^{-15.16t} + 0.028 e^{-183.24t} - \left[-5.46 \times 10^{-3} \times 4.73 e^{-15.16t} \right.$$


$$\left. - 0.066 \times (-0.391) e^{-183.24t} \right]$$

$$= -0.31 e^{-15.16t} + 0.002 e^{-183.24t} \quad A \quad t > 0$$

OR $i_L = \frac{1}{L} \int_0^t v(\tau) d\tau + i_L(0)$

$$\begin{aligned}
 i(t) &= \int_0^t [4.73e^{-15.16\tau} - 0.391e^{-183.24\tau}] d\tau - 310 \times 10^{-3} \\
 &= -0.31e^{-15.16t} + 0.002e^{-183.24t} - (-0.312 + 0.002) - \\
 &\quad 310 \times 10^{-3} \\
 &= -0.31e^{-15.16t} + 0.002e^{-183.24t} \text{ A } t > 0
 \end{aligned}$$

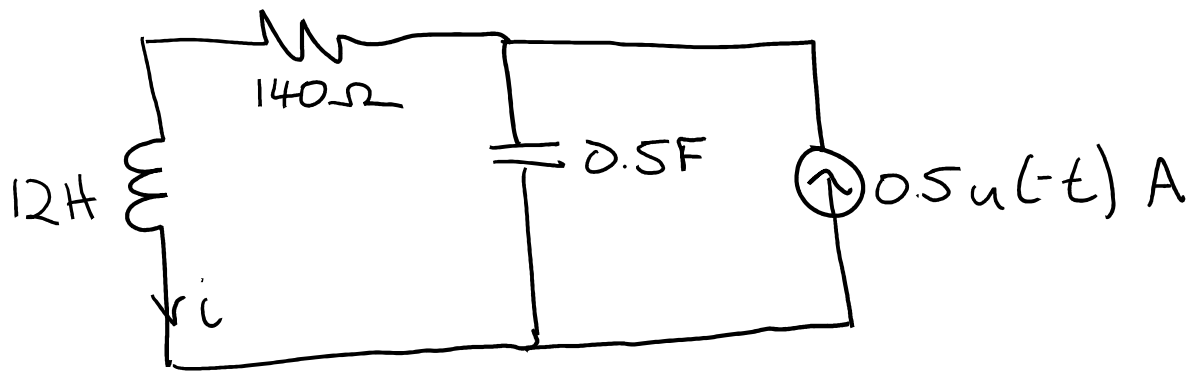Chapter 9, Ex 46: Source-free RLC Circuit




With reference to the circuit above, calculate a) α ; b) ω_0 ; c) $i(0^+)$; d) $\frac{di}{dt}\bigg|_{0^+}$

$$\begin{aligned} \text{a) } \alpha &= \frac{R}{2L} \\ &= \frac{140}{2 \times 12} \\ &= 5.83 \text{ s}^{-1} \end{aligned}$$


$$\begin{aligned} \text{b) } \omega_0 &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{12 \times 0.5}} \\ &= 0.41 \text{ rad/s} \end{aligned}$$

c) $t < 0$:

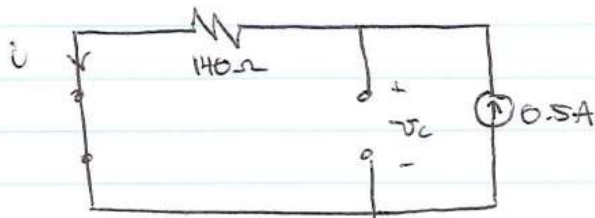

$$i(0^-) = 0.5 \text{ A} = i(0^+)$$

d) $t > 0$:

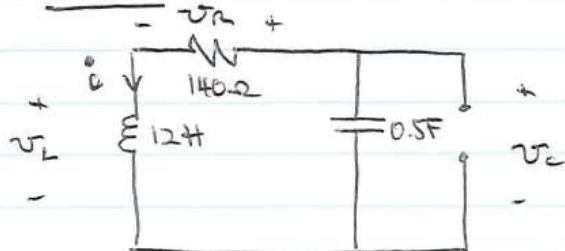

$$v_L = L \frac{di}{dt} = 12 \frac{di}{dt}$$

$$v_L(0^+) - v_C(0^+) + v_R(0^+) = 0$$

$$v_C(0^+) = v_C(0^-) = v_R(0^-) = 0.5 \times 140 \\ = 70V$$


$$v_R(0^+) = iR \\ = 0.5 \times 140 \\ = 70V$$

$$12 \frac{di}{dt} \Big|_{t=0} - 70 + 70 = 0$$

$$\frac{di}{dt} \Big|_{t=0} = 0$$

At Tutorial 6 – Marked Question (31st May 2019)


Chapter 9, Ex 50: Driven RLC Circuit

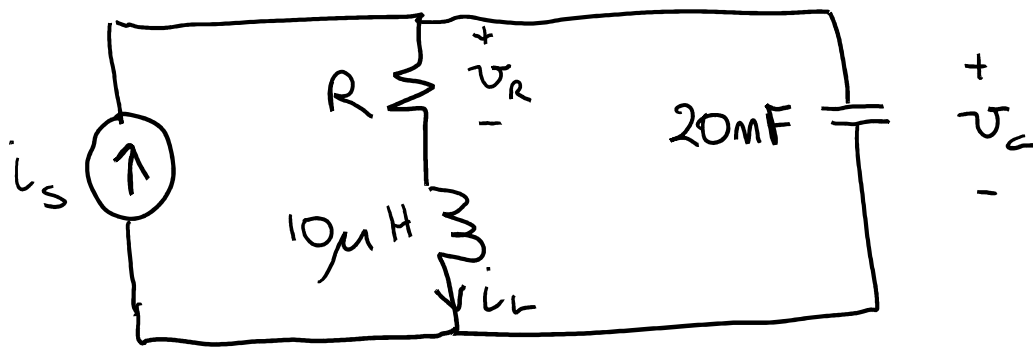

In the series circuit above, set $R = 1 \Omega$. a) Compute α and ω_0 . b) If $i_s = 3u(-t) + 2u(t)$ mA, determine $v_R(0^-)$, $i_L(0^-)$, $v_C(0^-)$, $v_R(0^+)$, $i_L(0^+)$, $v_C(0^+)$, $i_L(\infty)$, and $v_C(\infty)$.

$$\begin{aligned} \text{a) } \alpha &= \frac{R}{2L} = \frac{1}{2 \times 10 \times 10^{-6}} = 50 \times 10^3 \text{ s}^{-1} \\ \omega_0 &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10 \times 10^{-6} \times 20 \times 10^{-3}}} = 2.236 \times 10^3 \text{ rad/s} \end{aligned}$$

b) $t < 0$:

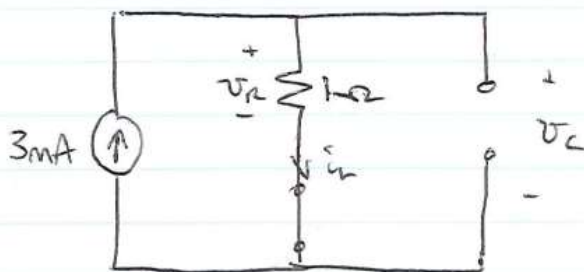


$$v_R = 3 \times 10^{-3} \times 1 = 3 \text{ mV}$$

$$i_L(0^-) = 3 \text{ mA}$$

$$v_C(0^-) = v_R(0^-) = 3 \text{ mV}$$

$t > 0$ (complete):

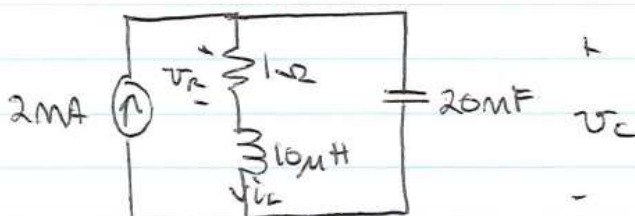


$$i_L(0^-) = i_L(0^+) = 3 \text{ mA}$$

$$v_R(0^+) = 3 \times 10^{-3} \times 1 = 3 \text{ mV}$$

$$v_C(0^+) = v_C(0^-) = 3 \text{ mV}$$

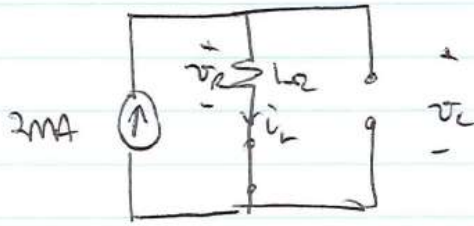At $t = \infty$, only the forced response is left, as the natural response $\rightarrow 0$ as $t \rightarrow \infty$:



$$i_L(\infty) = 2\text{mA}$$


$$v_L(\infty) = 2 \times 10^{-3} \times 1 \\ = 2\text{mV}$$




circuit for $t > 0$, forced response

At Tutorial 6 – Unmarked Questions (31st May 2019)

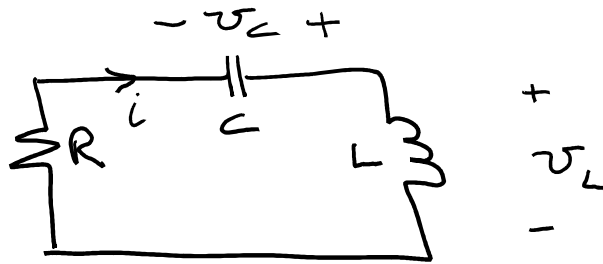Chapter 9, Ex 42: Source-free RLC Circuit



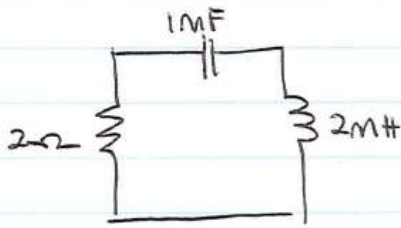Component values of $R = 2 \, \Omega$, $C = 1 \, \text{mF}$, and $L = 2 \, \text{mH}$ are used to construct the circuit represented above. If $v_C(0^-) = 1 \, \text{V}$ and no current initially flows through the inductor, calculate $i(t)$ at $t = 1 \, \text{ms}$, $2 \, \text{ms}$, and $3 \, \text{ms}$.



$$\begin{aligned}\alpha &= \frac{R}{2L} \\ &= \frac{2}{2 \times 2 \times 10^{-3}} \\ &= 500 \, \text{s}^{-1}\end{aligned}$$

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{2 \times 10^{-3} \times 1 \times 10^{-3}}} \\ &= 707 \, \text{rad/s}\end{aligned}$$

$\alpha < \omega_0 \quad \therefore \text{underdamped}$

$$\begin{aligned}\Rightarrow i(t) &= e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t) \\ &= e^{-500t} (B_1 \cos 500t + B_2 \sin 500t)\end{aligned}$$

$$\begin{aligned}\omega_d &= \sqrt{\omega_0^2 - \alpha^2} \\ &= \sqrt{707^2 - 500^2} \\ &= 500 \, \text{rad/s}\end{aligned}$$

$$i(0^+) = i(0^-) = 0 = B_1$$

$$\Rightarrow i(t) = B_2 e^{-500t} \sin 500t$$

$$v_C(0^-) = v_C(0^+) = 1 \, \text{V}$$

$$\begin{aligned}v_L &= L \frac{di}{dt} \\ &= 2 \times 10^{-3} (-500 B_2 e^{-500t} \sin 500t + 500 B_2 e^{-500t} \cos 500t)\end{aligned}$$

$$\begin{aligned}v_L(0) &= 2 \times 10^{-3} (500 B_2) \\ &= B_2\end{aligned}$$

$$v_L - v_R - v_C = 0$$

$$b_2 - 0 - 1 = 0$$

$$b_2 = 1$$


$$i(t) = e^{-500t} \sin 500t + A \quad t \geq 0$$

$$i(1\text{ms}) = 0.291 \text{ A}$$

$$i(2\text{ms}) = 0.310 \text{ A}$$


$$i(3\text{ms}) = 0.223 \text{ A}$$

Chapter 9, Ex 52: Forced RLC Circuit

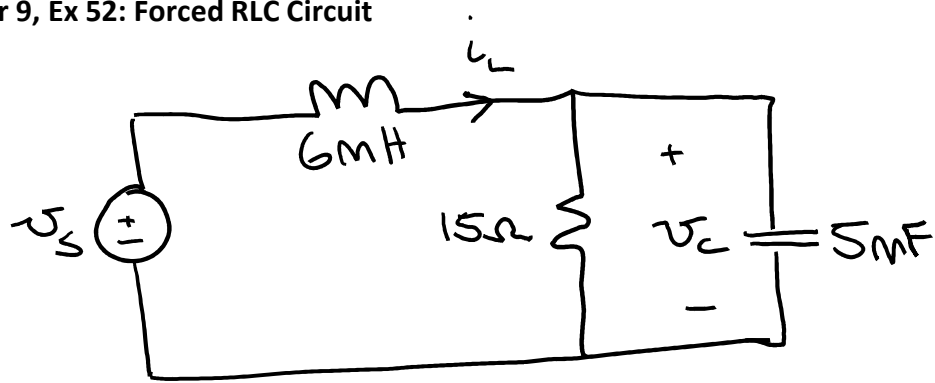

Consider the circuit depicted above. If $v_s(t) = -8 + 2u(t)$ V, determine:

a) $v_C(0^+)$

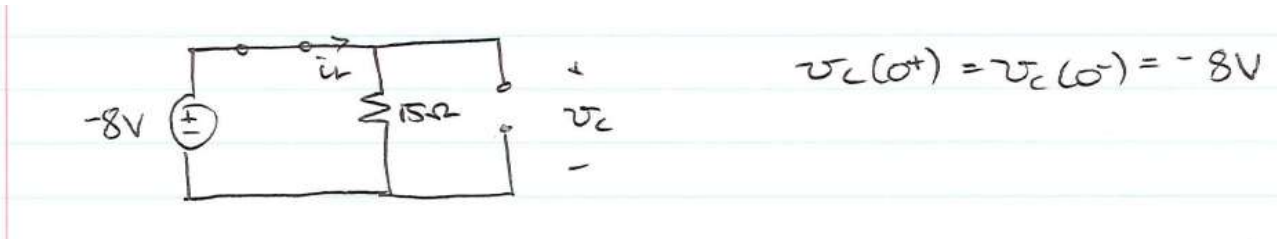


b) $i_L(0^+)$

$$i_L(0^+) = i_L(0^-) = \frac{-8}{15} = -0.53 \text{ A}$$

c) $v_C(\infty)$

forced response, $t > 0$:

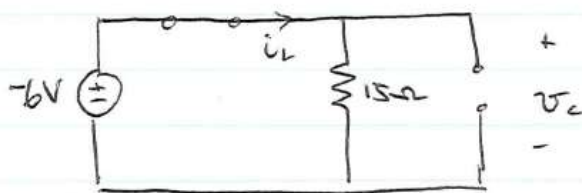


$$v_C(\infty) \Rightarrow \text{forced response only} = -6V$$

d) $v_C(t = 150\text{ms})$

$v_C(150\text{ms}) \Rightarrow$ need complete response

natural response, $t > 0$:

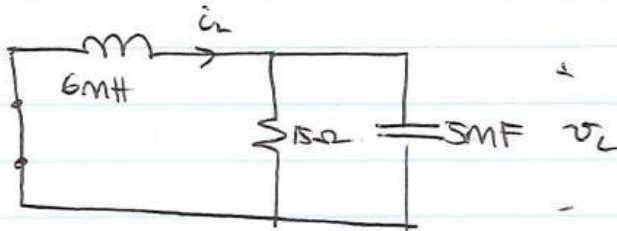

$$\begin{aligned}\alpha &= \frac{1}{2RC} \\ &= \frac{1}{2 \times 15 \times 5 \times 10^{-3}} \\ &= 6.67 \text{ s}^{-1}\end{aligned}$$

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{6 \times 10^{-3} \times 5 \times 10^{-3}}} \\ &= 182.6 \text{ rad/s}\end{aligned}$$

$$\Rightarrow \alpha < \omega_0 \quad \therefore \text{underdamped}$$

$$\therefore v_{C,n} = e^{-\alpha t} (B_1 \cos \omega_\alpha t + B_2 \sin \omega_\alpha t)$$

$$\begin{aligned}\omega_\alpha &= \sqrt{\omega_0^2 - \alpha^2} \\ &= \sqrt{182.6^2 - 6.67^2} \\ &= 182.5 \text{ rad/s}\end{aligned}$$

$$v_{C,n} = e^{-6.67t} (B_1 \cos 182.5t + B_2 \sin 182.5t)$$

$$\begin{aligned}v_C(t) &= v_{C,p} + v_{C,n} \\ &= -6 + e^{-6.67t} (B_1 \cos 182.5t + B_2 \sin 182.5t)\end{aligned}$$

$$\begin{aligned}v_C(0) &= -6 + B_1 = -8 \\ B_1 &= -2\end{aligned}$$

$$\begin{aligned}\frac{dv_C}{dt} &= -6.67 e^{-6.67t} (-2 \cos 182.5t + B_2 \sin 182.5t) \\ &\quad + e^{-6.67t} (-365 \sin 182.5t + 182.5 B_2 \cos 182.5t)\end{aligned}$$

$$\begin{aligned}\left. \frac{dv_C}{dt} \right|_{t=0} &= -6.67 \times -2 + 182.5 B_2 \\ &= 182.5 B_2 + 13.33\end{aligned}$$

$$i_C = C \frac{dv}{dt}$$

$$i_C + i_R - i_L = 0$$

at $t=0$:

$$5 \times 10^{-3} (182.5 B_2 + 13.33) + \left(\frac{-8}{15} \right) - (-0.53) = 0$$

$$0.9125 B_2 + 0.067 - 0.53 + 0.53 = 0$$

$$B_2 = -0.07$$

$$v_C(t) = -6 + e^{-6.67t} (-2 \cos 182.5t - 0.07 \sin 182.5t) \text{ V } t > 0$$

$$v_C(150 \text{ ms}) = -5.56 \text{ V}$$