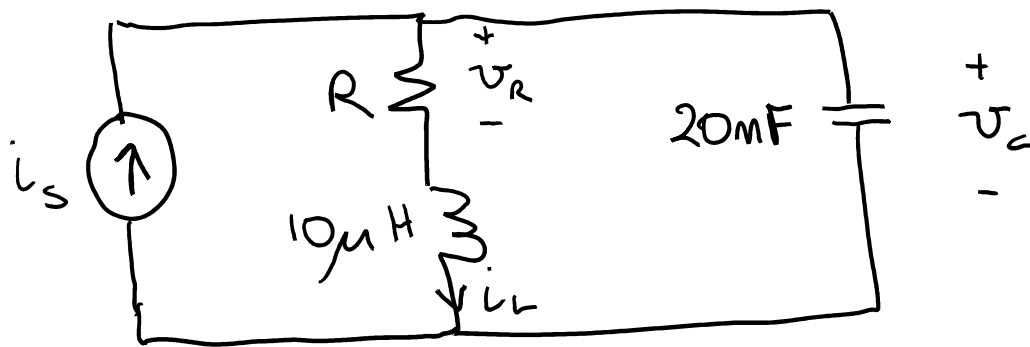


At Tutorial 6 – Marked Question (31st May 2019)


Chapter 9, Ex 50: Driven RLC Circuit



In the series circuit above, set $R = 1\ \Omega$. a) Compute α and ω_0 . b) If $i_s = 3u(-t) + 2u(t)$ mA, determine $v_R(0^-)$, $i_L(0^-)$, $v_C(0^-)$, $v_R(0^+)$, $i_L(0^+)$, $v_C(0^+)$, $i_L(\infty)$, and $v_C(\infty)$.


At Tutorial 6 – Unmarked Questions (31st May 2019)

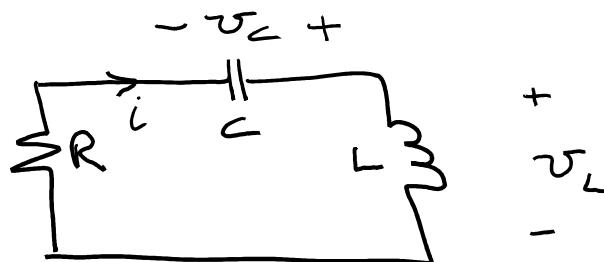Chapter 9, Ex 42: Source-free RLC Circuit



Component values of $R = 2\ \Omega$, $C = 1\ \text{mF}$, and $L = 2\ \text{mH}$ are used to construct the circuit represented above. If $v_C(0^-) = 1\ \text{V}$ and no current initially flows through the inductor, calculate $i(t)$ at $t = 1\ \text{ms}$, 2ms , and 3ms .

Chapter 9, Ex 52: Forced RLC Circuit

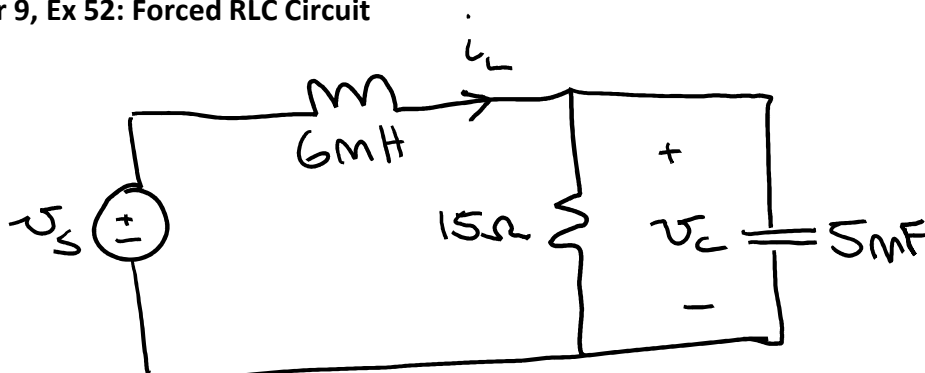

Consider the circuit depicted above. If $v_s(t) = -8 + 2u(t)$ V, determine:

- $v_C(0^+)$
- $i_L(0^+)$
- $v_C(\infty)$
- $v_C(t = 150\text{ms})$